

Cybersecurity for IoT – FPGA Introduction

Department of Electrical, Computer and Biomedical
Engineering of University of Pavia

Master of Science Program in
Computer Engineering

Instructor: Paris Kitsos

<http://diceslab.cied.teiwest.gr>


E-mail: pkitsos@teimes.gr

Pavia 2018

This lecture is based on “FPGA – based System Design”, book by Wayne Wolf

Elements of an FPGA fabric

- Logic.
- Interconnect.
- I/O pins.

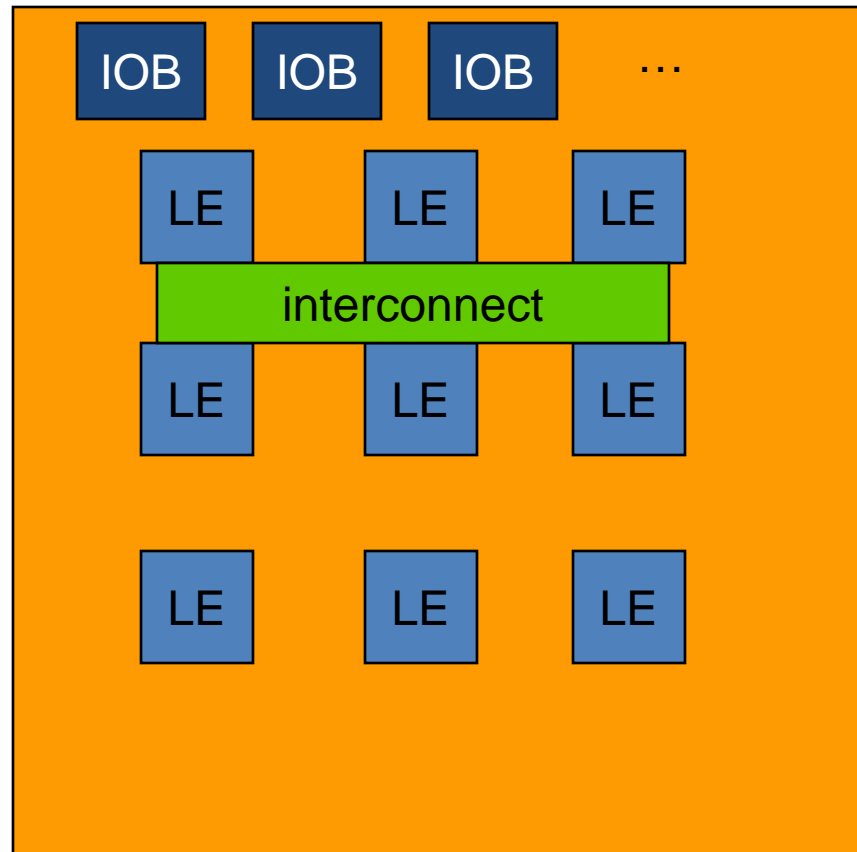

Terminology


- Configuration: bits that determine logic function + interconnect.
- CLB: combinational logic block = logic element (LE).
- LUT: Lookup table = SRAM used for truth table.
- I/O block (IOB): I/O pin + associated logic and electronics.

Logic element

- Programmable:
 - Input connections.
 - Internal function.
- Generally includes register.
- May provide specialized logic.
 - Adder carry chain.

Example logic element


- Lookup table:

 


a	b	out
0	0	0 1
0	1	0 0 1 0
1	0	0 1
1	1	

Placement

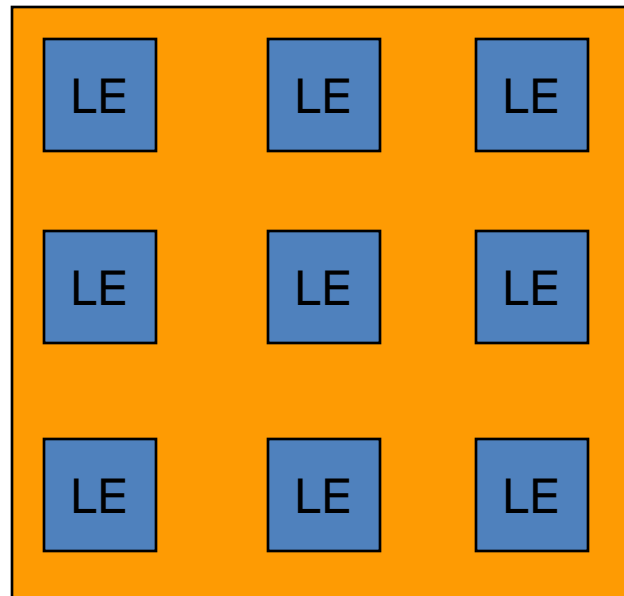
- Where do we put each piece of logic in the array of logic elements?




Programmable interconnection point...

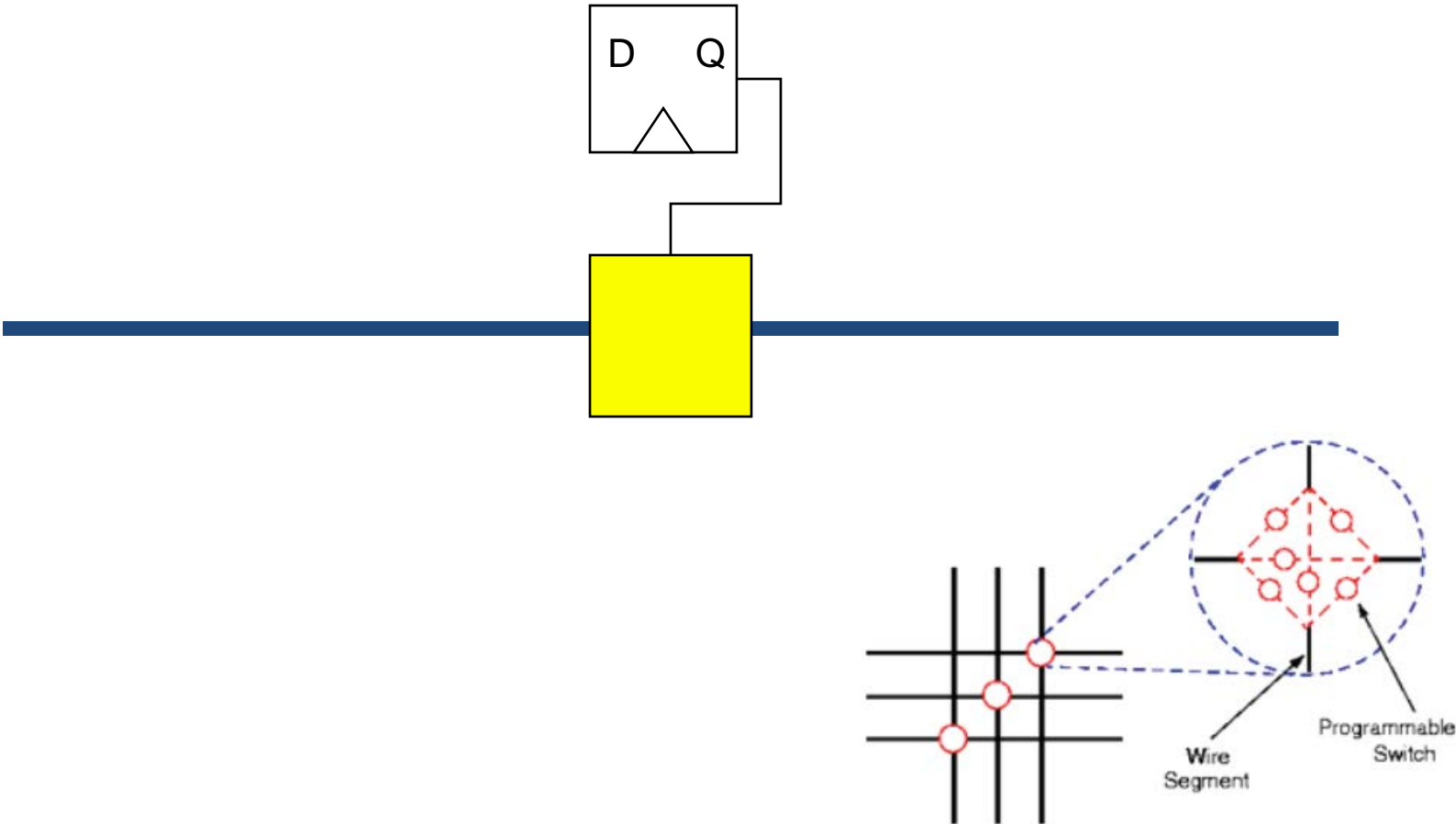


...Programmable interconnection point

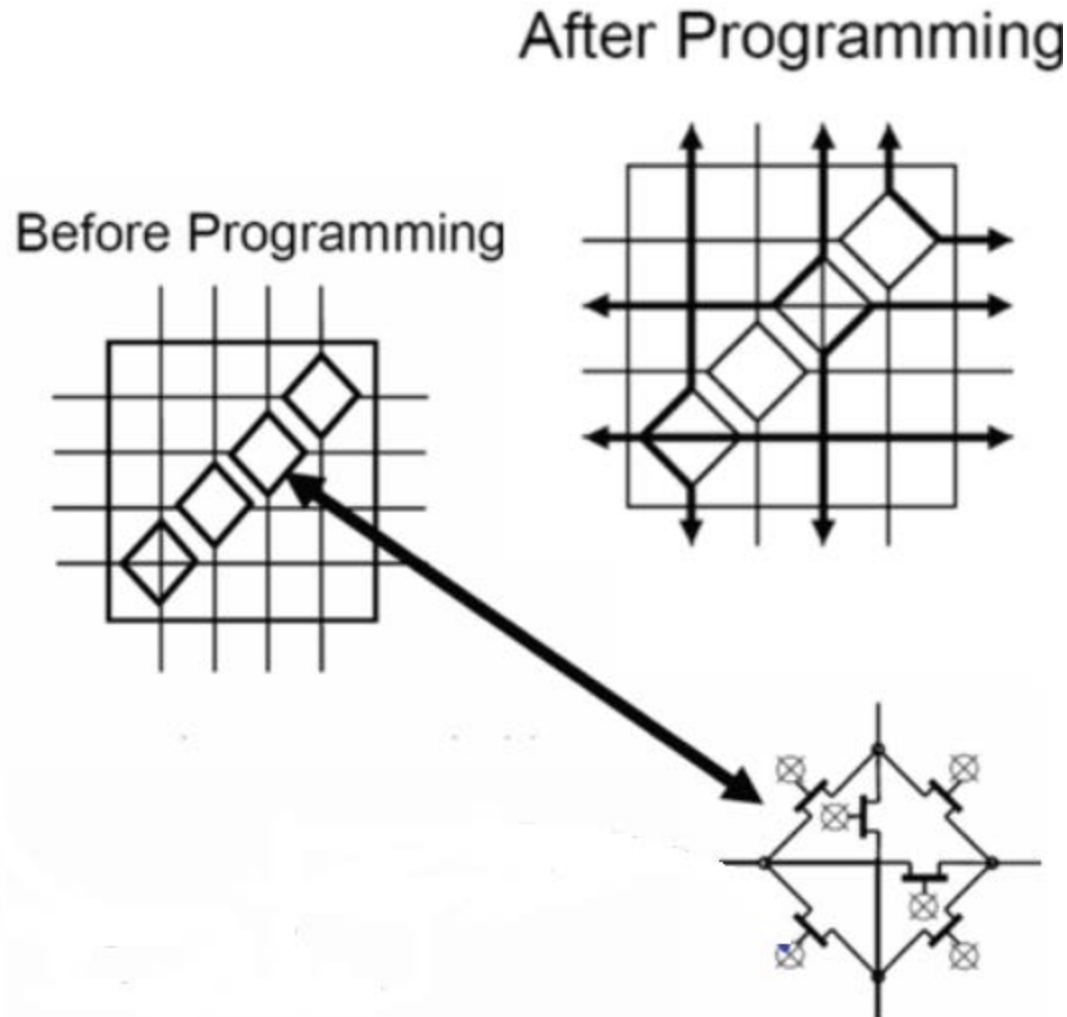


Programmable wiring paths

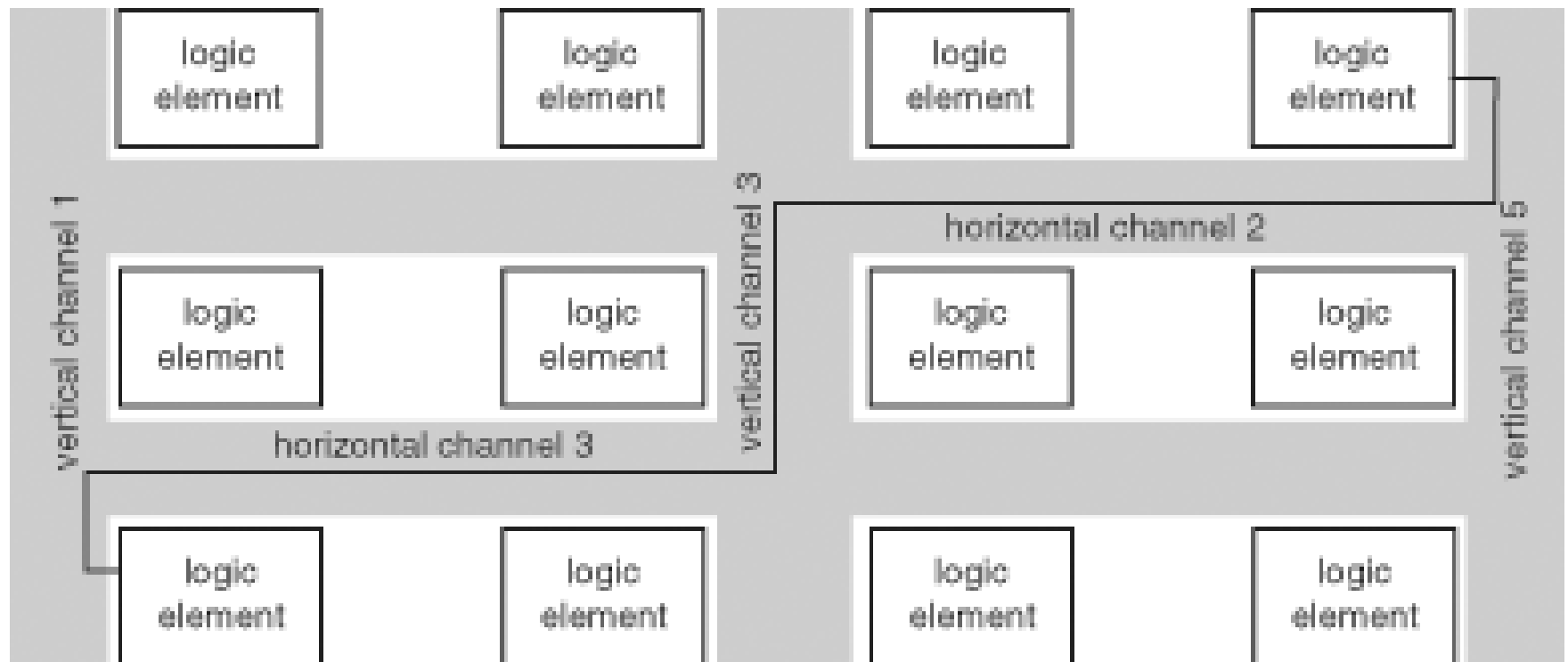


Choosing a path

 

Segmented wiring

 

Offset segments

 

I/O

- Fundamental selection: input, output, three-state?
- Additional features:
 - Register.
 - Voltage levels.
 - Slew rate.

Programming technologies

- SRAM.
 - Can be programmed many times.
 - Must be programmed at power-up.
- Antifuse.
 - Programmed once.
- Flash.
 - Similar to SRAM but using flash memory.

Configuration

- Must set control bits for:
 - LE.
 - Interconnect.
 - I/O blocks.
- Usually configured off-line.
 - Separate burn-in step (antifuse).
 - At power-up (SRAM).

SRAM-based FPGAs

- Program logic functions, interconnect using SRAM.
- Advantages:
 - Re-programmable;
 - dynamically reconfigurable;
 - uses standard processes.
- Disadvantages:
 - SRAM burns power.
 - Possible to steal, disrupt configuration bits.

Logic elements


- Logic element includes combinational function + register(s).
- Use SRAM as lookup table for combinational function.

Evaluation of SRAM-based LUT

- N-input LUT can handle function of 2^n inputs.
- All logic functions take the same amount of space.
- All functions have the same delay.
- SRAM is larger than static gate equivalent of function.

Registers in logic elements

 
- Register may be selected into the circuit:




Other LE features

- Multiple logic functions in an LE.
- Addition logic:
 - carry chain.
- Partitioned lookup tables.


Logic correspondence in a LUT...

 

...Logic correspondence in a LUT...

 


...Logic correspondence in a LUT

 

Configurable Logic Element (or Logic Element)...

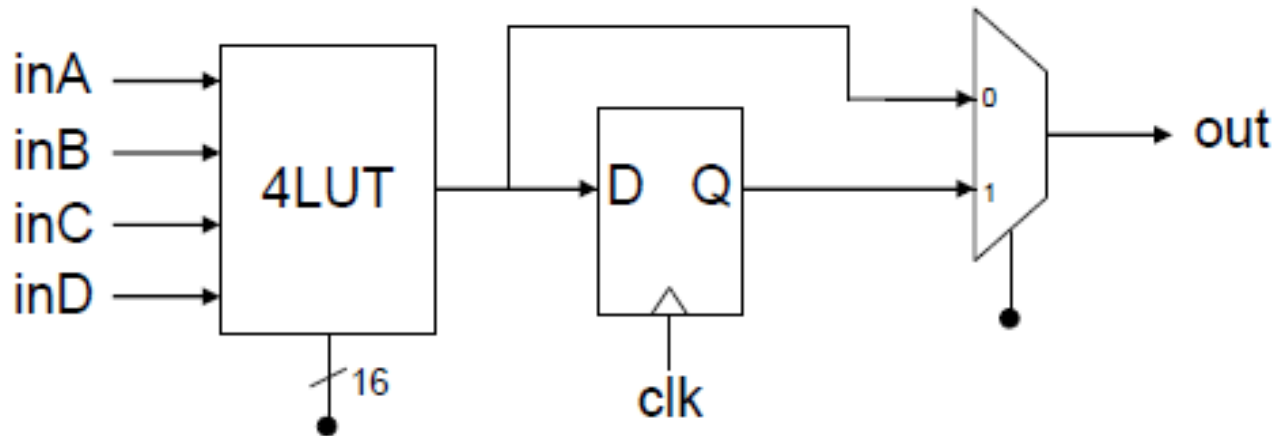
- Consists of a LUT, a Flip-flop and a Multiplexer




...Configurable Logic Element (or

• Two outputs Logic Element)...

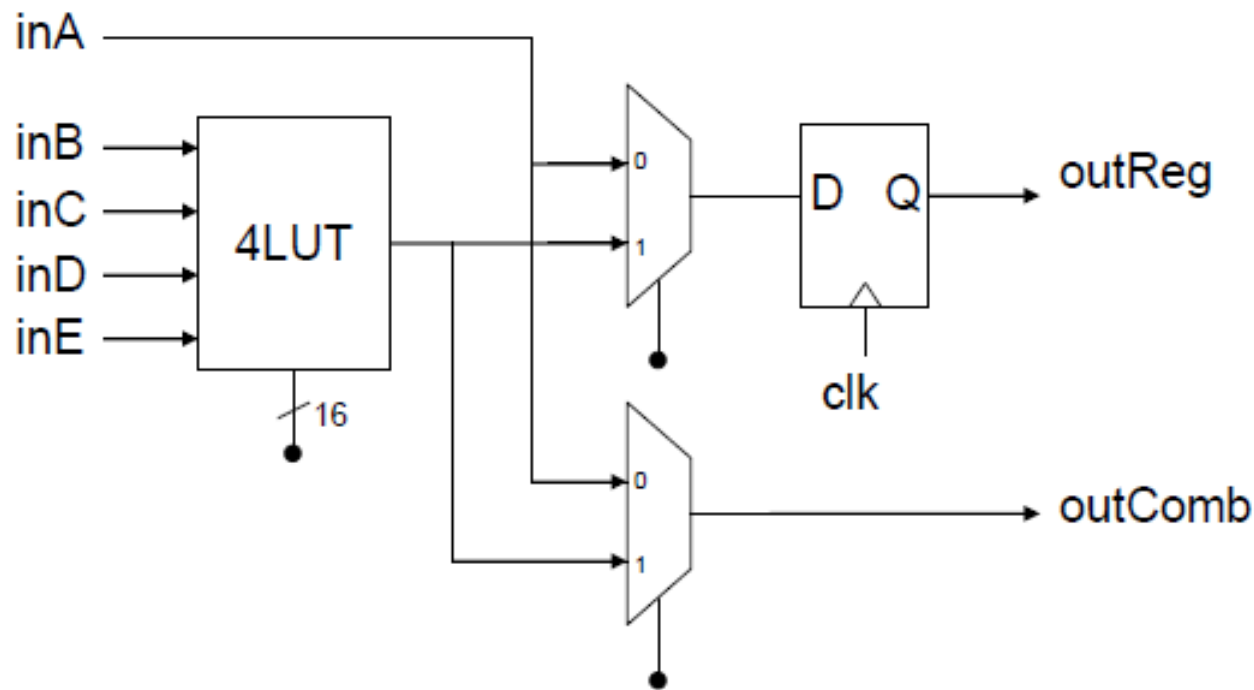
- Output of the combinatorial logic
- Output of a register




An Example of Configuration

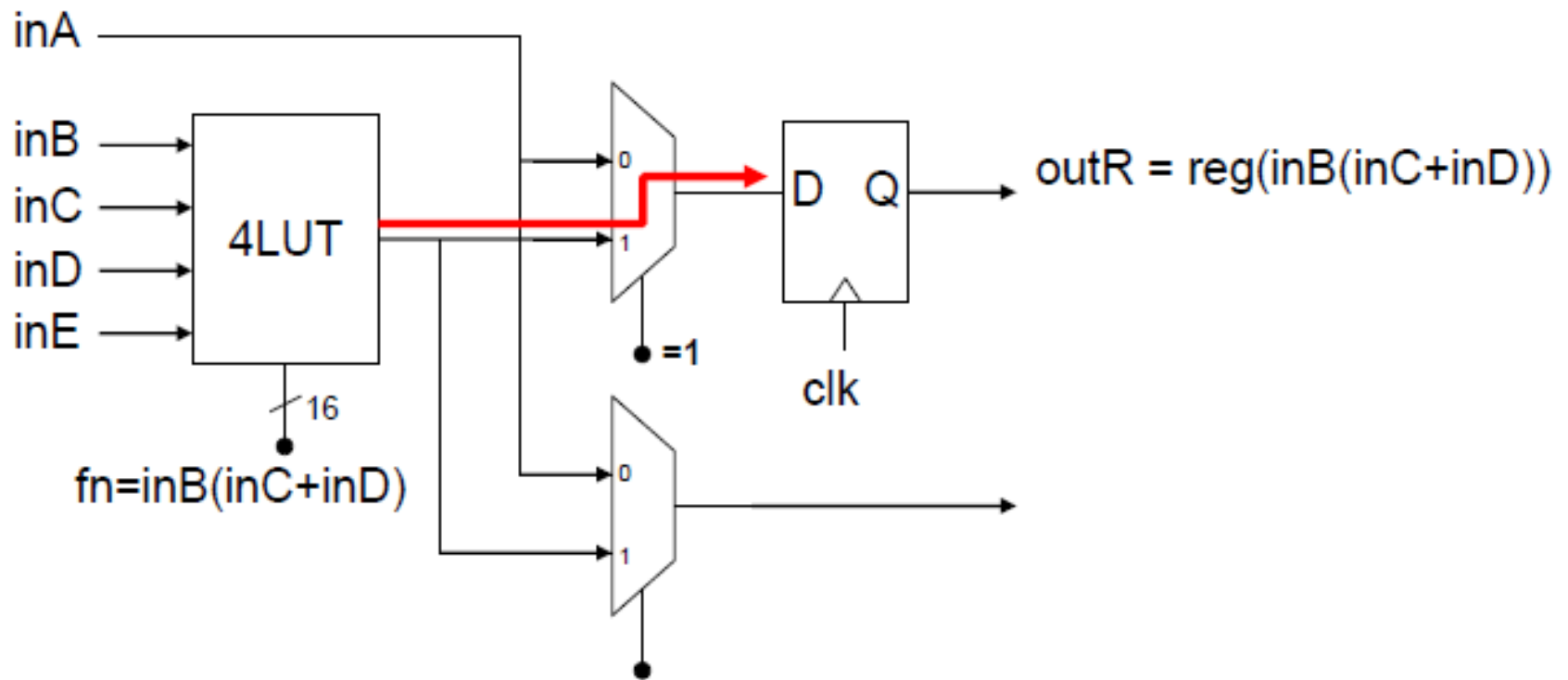

Another Example of Configuration

 


One More Example of a Configuration

 


 Example...

- Let us consider we want to generate the signals N, Z, P according to the below logic




... Example...

 

LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$ LUT #8: $F3 = D5$ έξοδος N

LUT #7: $F2 = F1 \cdot D4' \cdot D5'$ έξοδος Z LUT #9: $F4 = Z' \cdot N'$ έξοδος P


...Example...

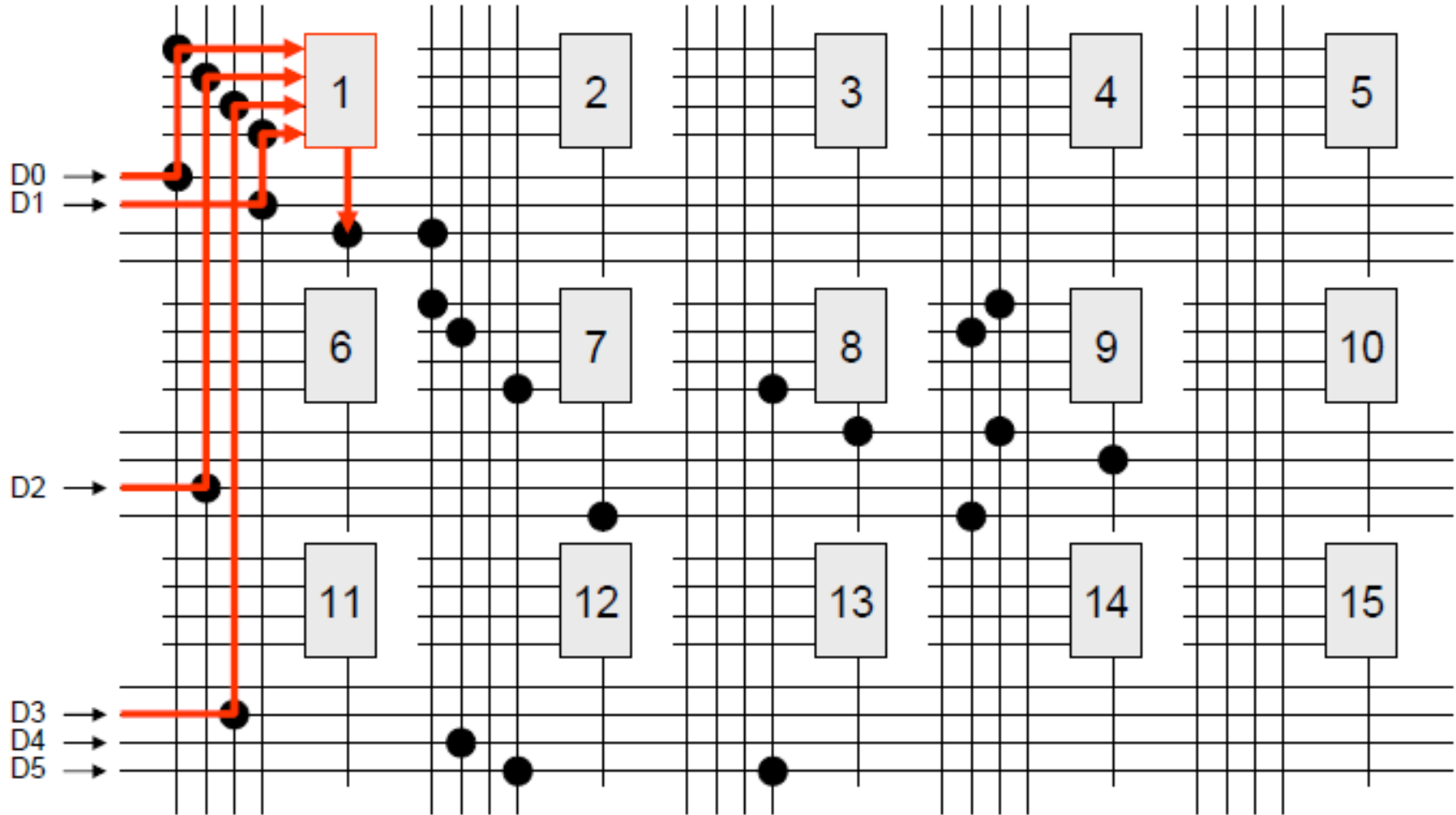

LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$ LUT #8: $F3 = D5$ έξοδος N

LUT #7: $F2 = F1 \cdot D4' \cdot D5'$ έξοδος Z LUT #9: $F4 = Z' \cdot N'$ έξοδος P


... Example ...

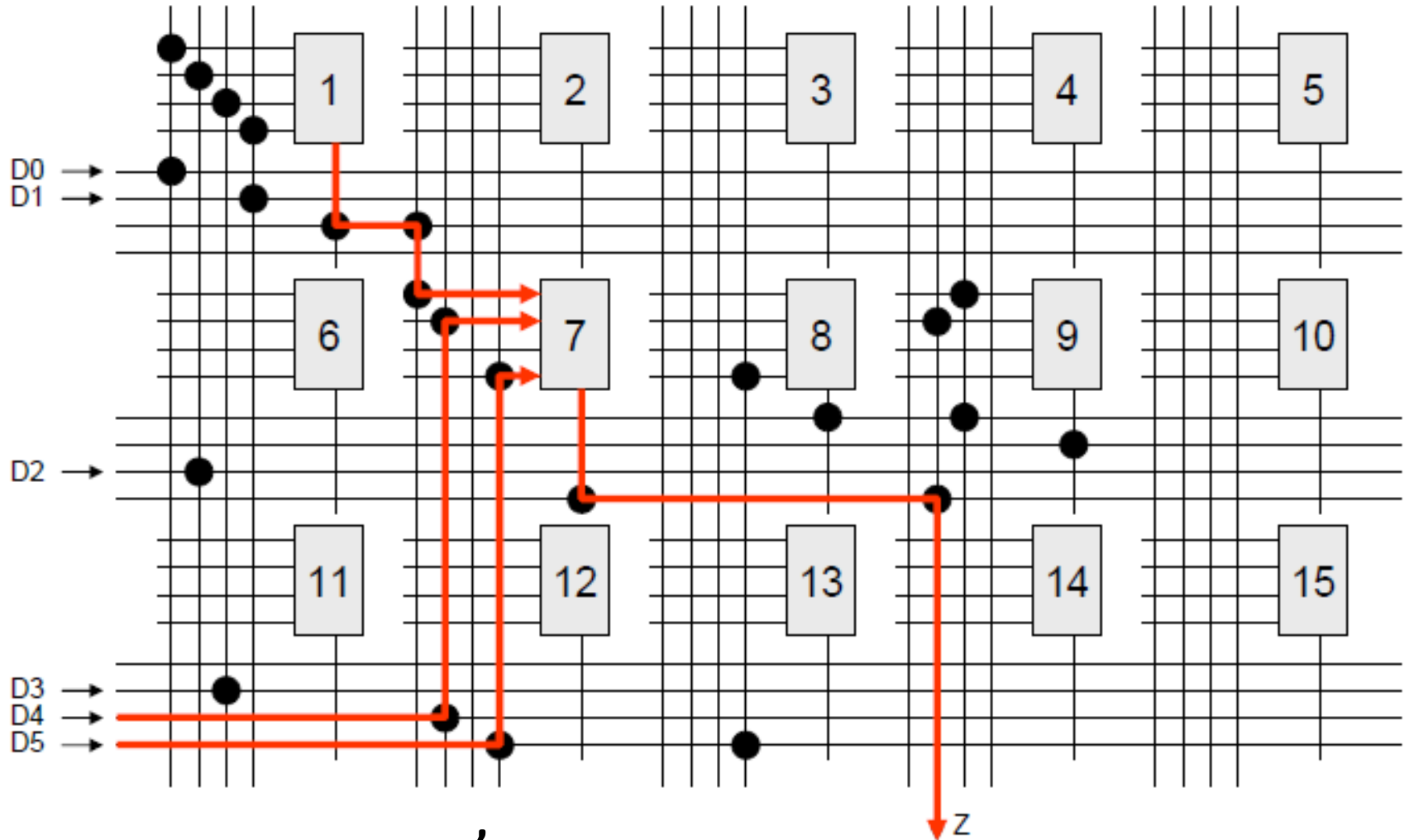

LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$ LUT #8: $F3 = D5$ output N

LUT #7: $F2 = F1 \cdot D4' \cdot D5'$ output Z LUT #9: $F4 = Z' \cdot N'$ output P

Example

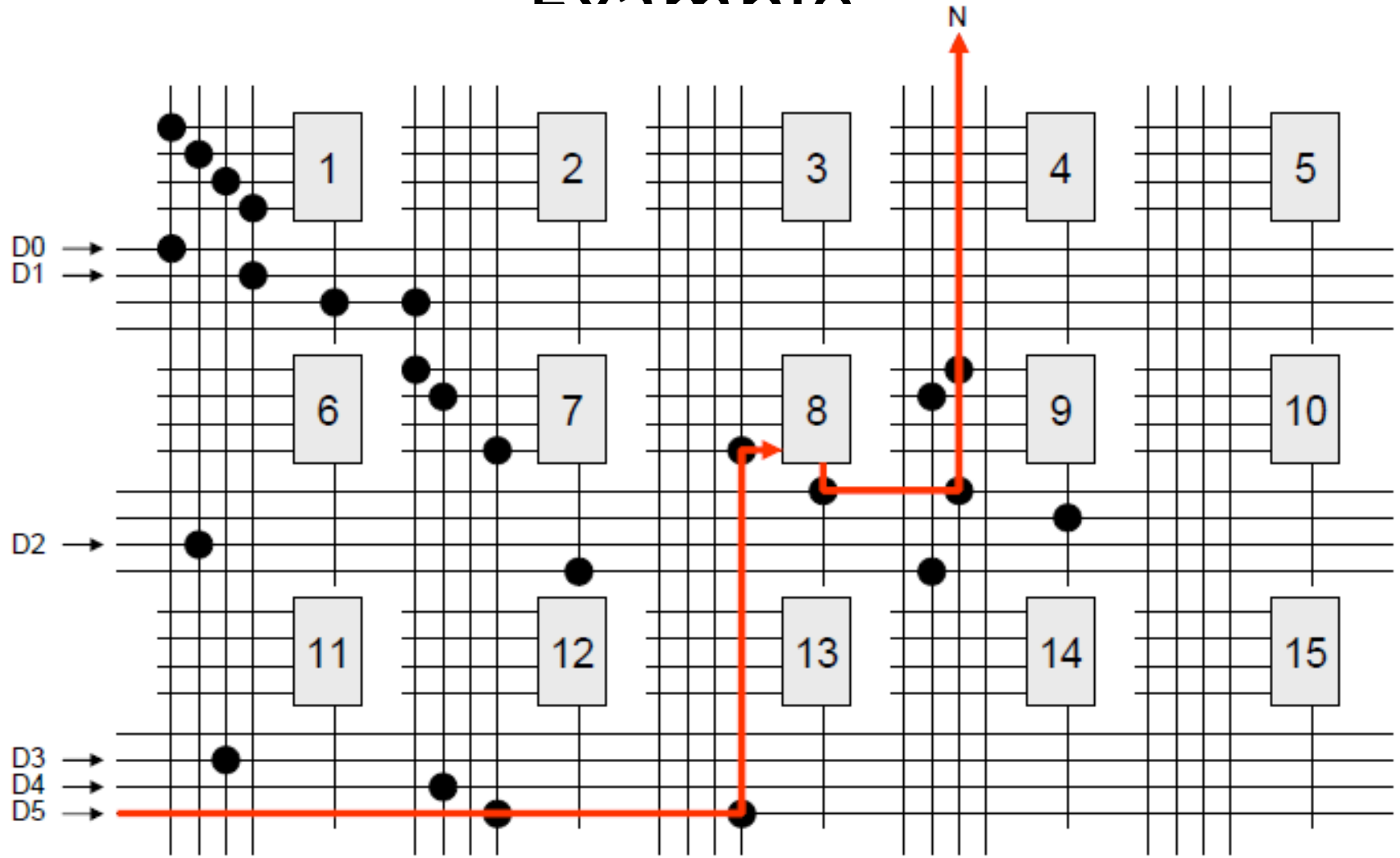


LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #8: $F3 = D5$ output N

LUT #7: $F2 = F1 \cdot D4' \cdot D5'$ output Z

LUT #9: $F4 = Z' \cdot N'$ output P

... Example

 

LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$ LUT #8: $F3 = D5$ output N

LUT #7: $F2 = F1 \cdot D4' \cdot D5'$ output Z LUT #9: $F4 = Z' \cdot N'$ output P

Questions??