

# Cybersecurity for IoT – Secure Hardware

Department of Electrical, Computer and Biomedical  
Engineering of University of Pavia

Master of Science Program in  
Computer Engineering

Instructor: Paris Kitsos

<http://diceslab.cied.teiwest.gr>


E-mail: [pkitsos@teimes.gr](mailto:pkitsos@teimes.gr)

Pavia 2018


- **Part 1 – Pipelining and Retiming**

# Delay of a Design

Delay = latency x clock period

 


# Minimum Clock Period...

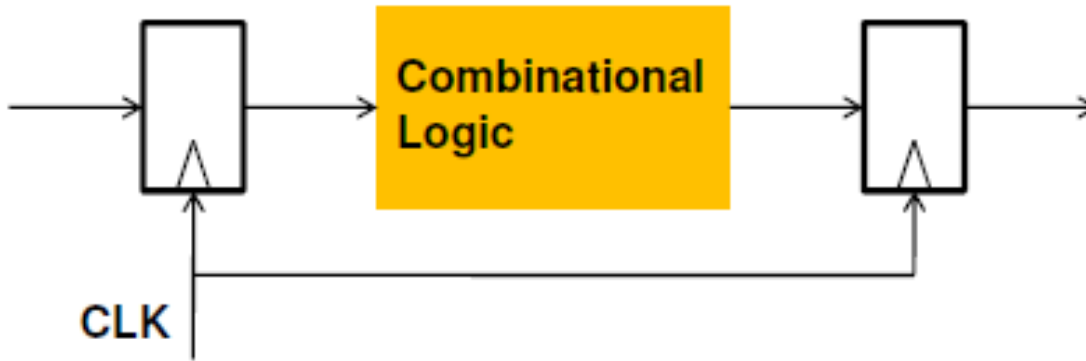


$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$

# ...Minimum Clock Period...

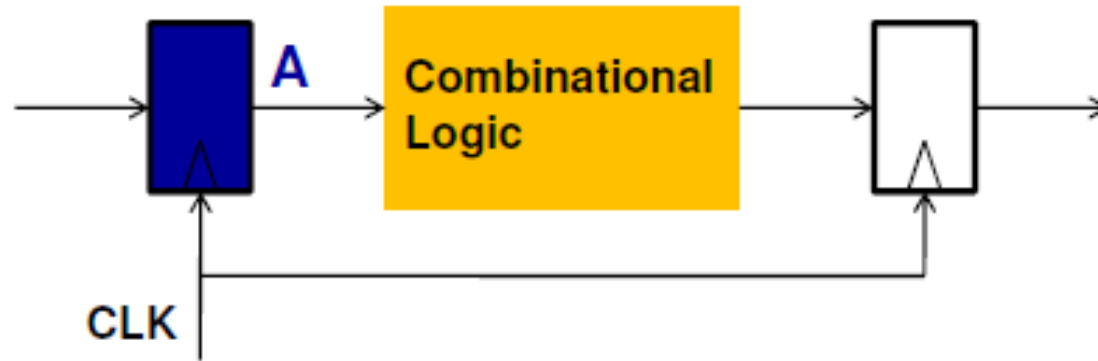


This is the time need for the output of a flip-flop to switch to a new value after a clock edge has occurred
 
$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$




# ...Minimum Clock Period...

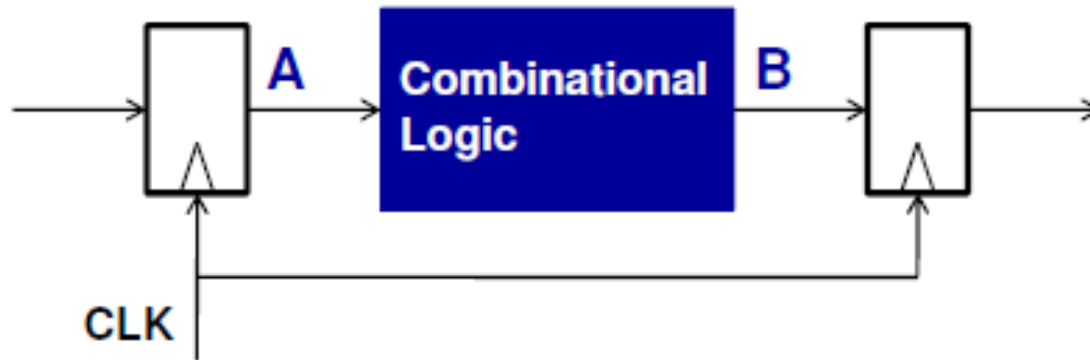


$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$

 
This is the time need for the logic to calculate a new output. Depends on the gates and wires




# ...Minimum Clock Period...

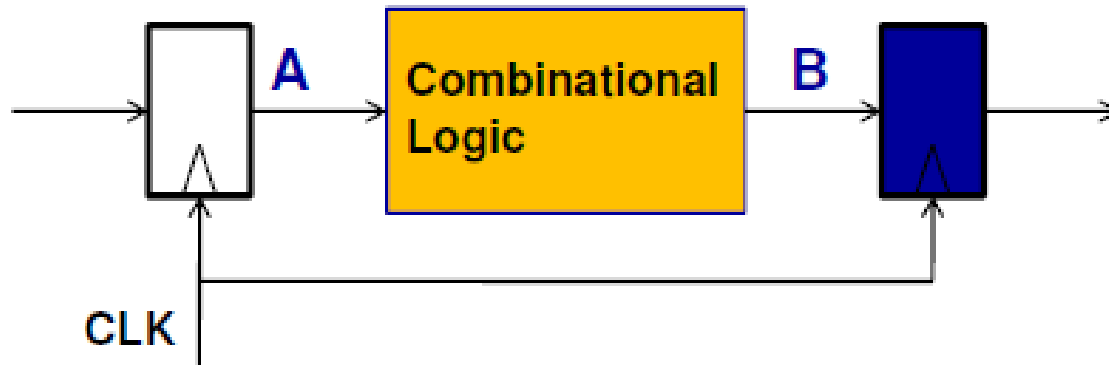

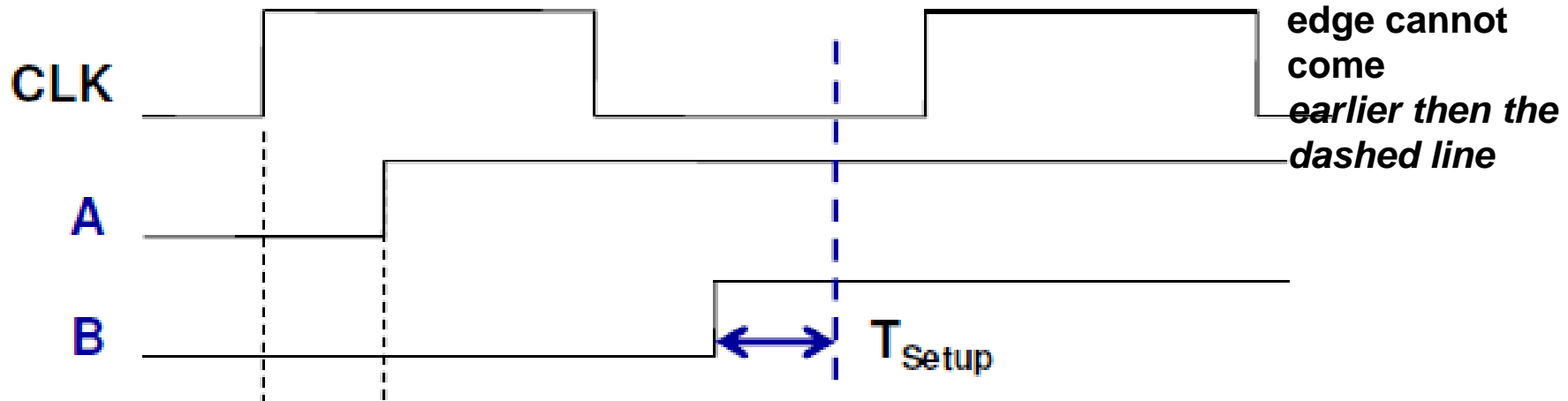
$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$



# ...Minimum Clock Period...

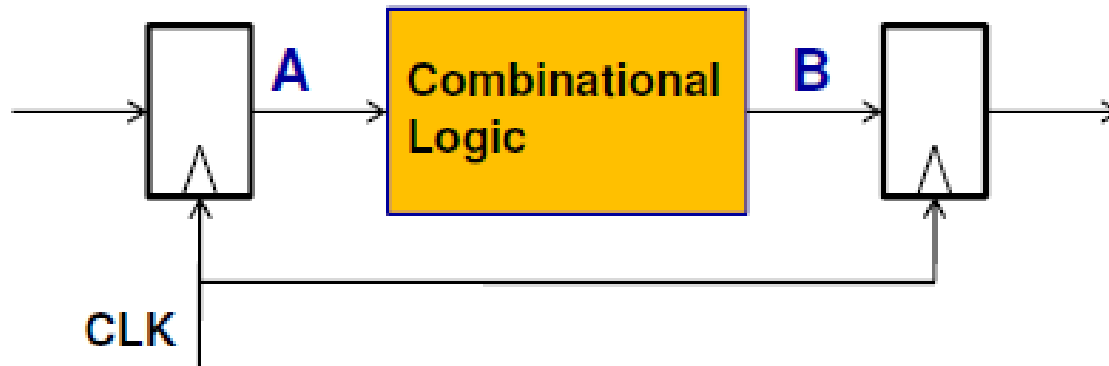

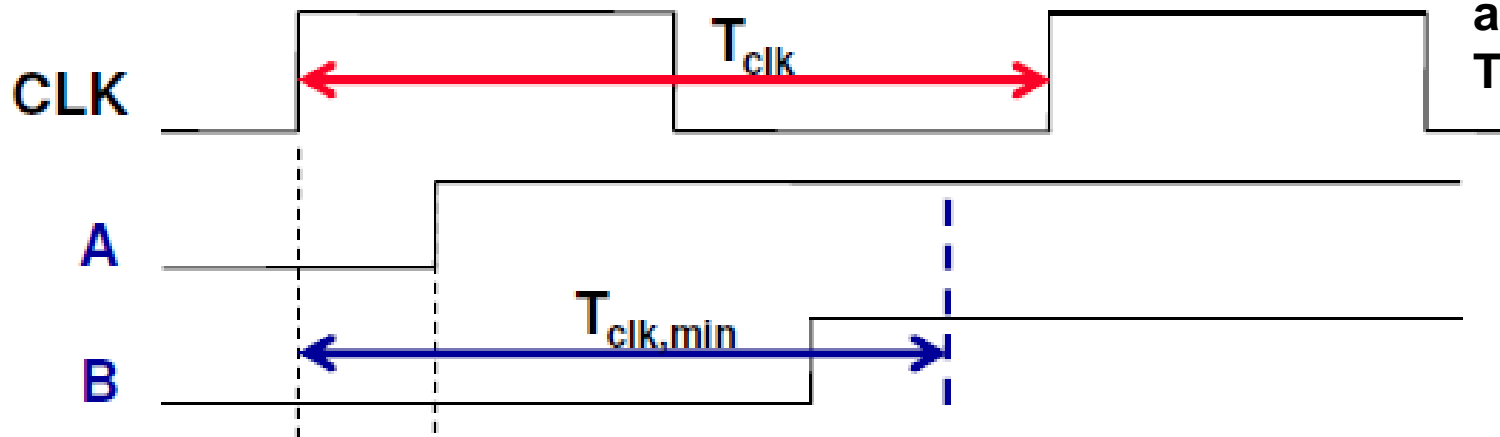
$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$



In this case, the timing of the system is OK, since the actual  $T_{\text{clk}} > T_{\text{clk,min}}$




# ...Minimum Clock Period...

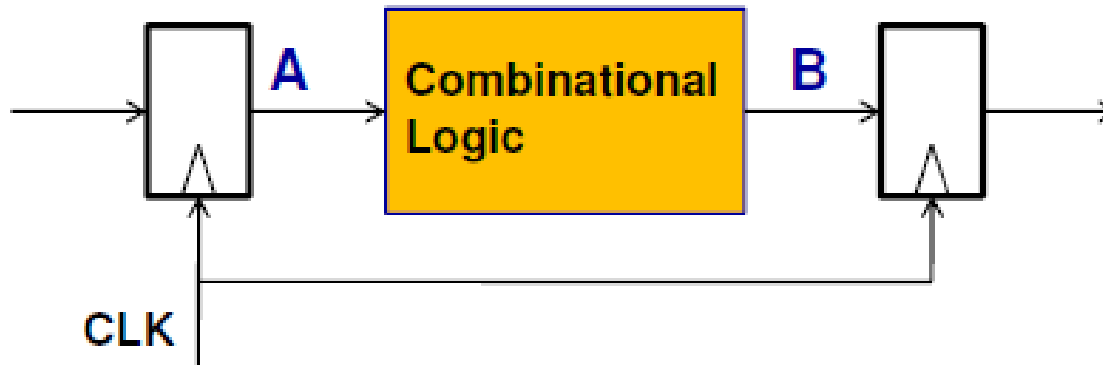


$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$

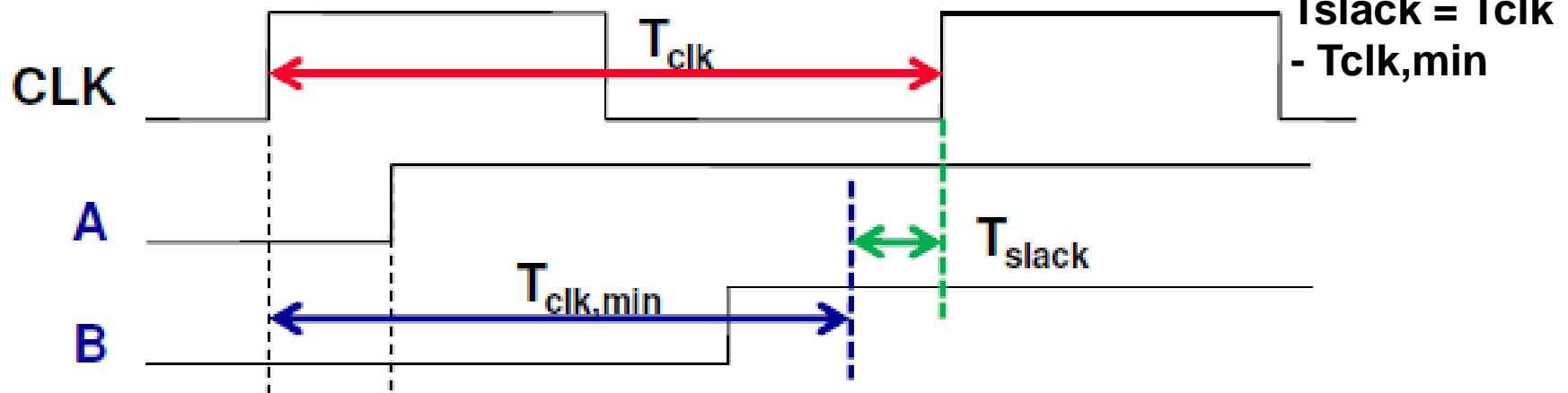
The margin between the actual clock period and the minimal clock period is called *slack*.



# ...Minimum Clock Period...

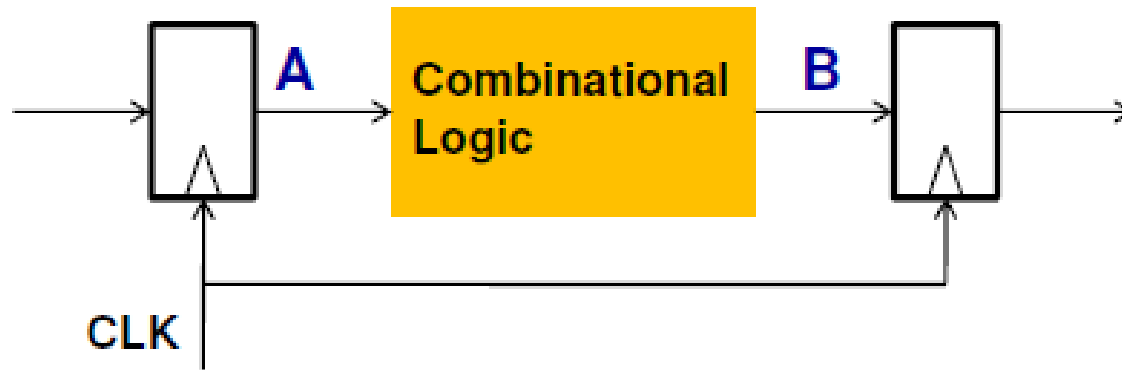

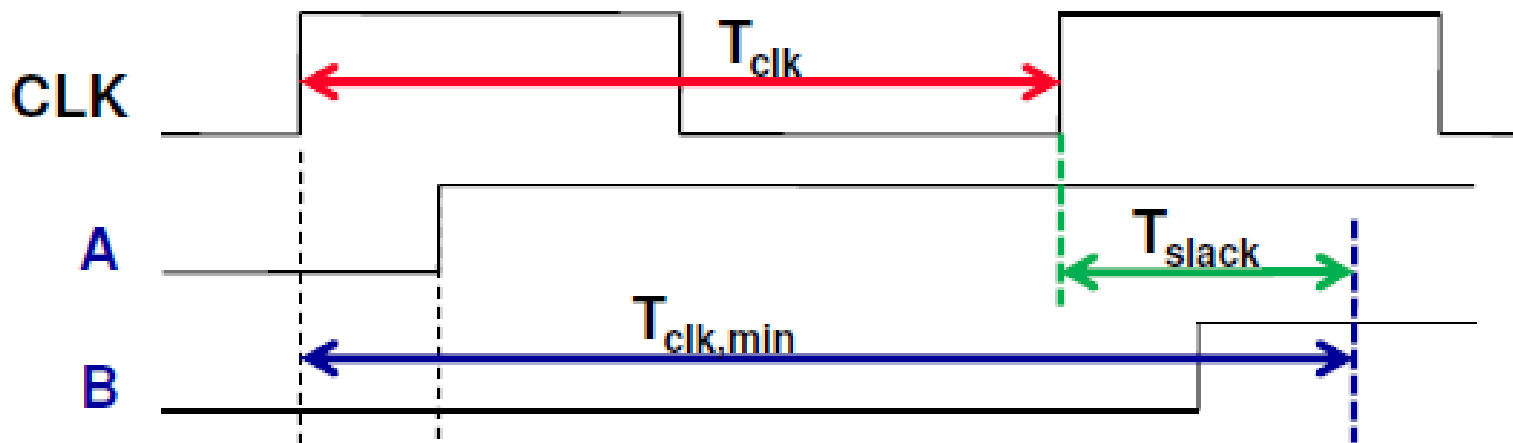
$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$



If the *slack is negative*, the system has a *timing violation*. This system will not perform as expected, since its clock frequency is too high.

# ...Minimum Clock Period...

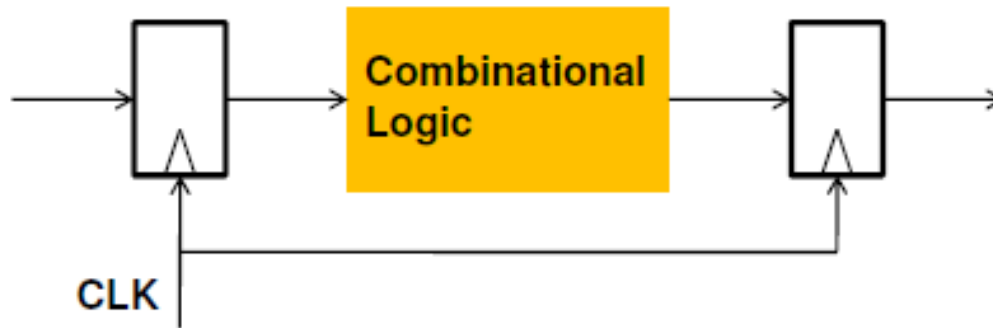

$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$


Once the technology is chosen,  $T_{\text{clk} \rightarrow \text{Q}}$  and  $T_{\text{setup}}$  are fixed.

An example from the Xilinx device datasheet is shown on the right.

Table 97: CLB (SLICEM) Timing

Symbol	Description	Speed Grade				Units
		-5		-4		
		Min	Max	Min	Max	
<b>Clock-to-Output Times</b>						
$T_{\text{COQ}}$	When reading from the FFX (FFY) Flip-Flop, the time from the active transition of the CLK input to data appearing at the XQ (YQ) output	-	0.52	-	0.60	ns
<b>Setup Times</b>						
$T_{\text{AS}}$	Time from the setup of data at the F or G input to the active transition of the CLK input of the CLB	0.46	-	0.52	-	ns
$T_{\text{DICK}}$	Time from the setup of data at the BX or BY input to the active transition of the CLK input of the CLB	0.32	-	0.36	-	ns
<b>Hold Times</b>						
$T_{\text{AH}}$	Time from the active transition of the CLK input to the point where data is last held at the F or G input	0	-	0	-	ns
$T_{\text{CKDH}}$	Time from the active transition of the CLK input to the point where data is last held at the BX or BY input	0	-	0	-	ns

# ...Minimum Clock Period

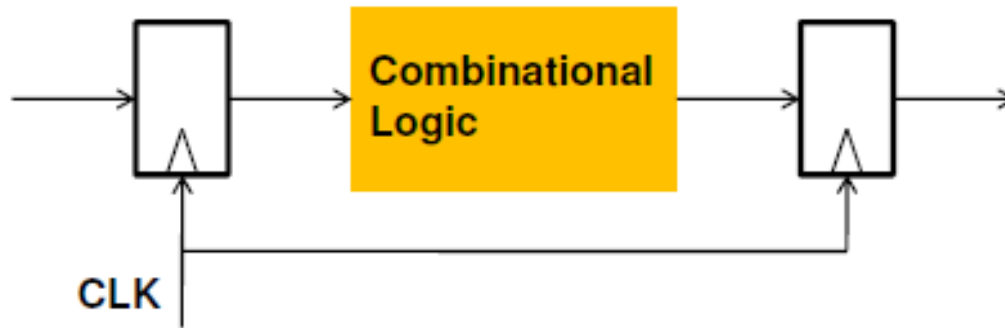


$$T_{\text{clk,min}} = T_{\text{clk} \rightarrow \text{Q}} + T_{\text{Logic}} + T_{\text{Routing}} + T_{\text{Setup}}$$

However, even after the technology is chosen, the designer can *still influence T<sub>logic</sub> and T<sub>routing</sub>* by making modifications to the HDL code.

Thus, if we want to decrease the minimum clock period, we need to consider these terms.
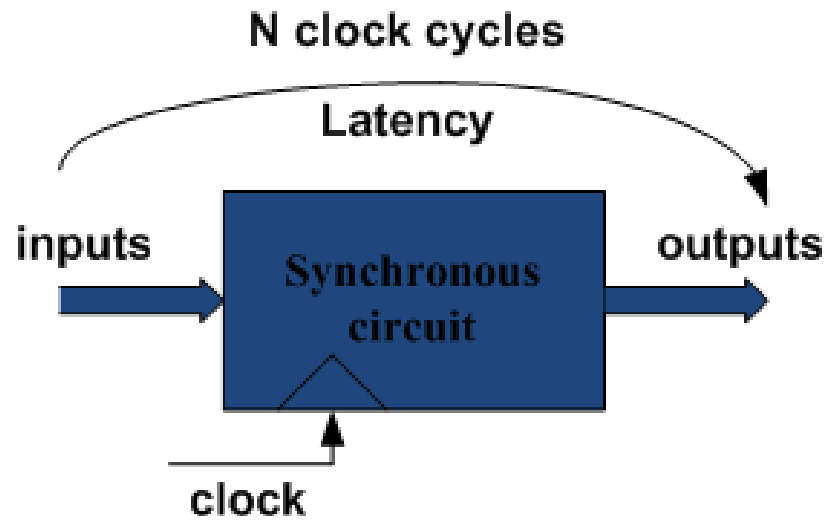
# Minimization of Delay

Delay = latency (clock cycles) x clock period




## Parallel Computations

Reduce the # cycles required

## Pipelining and Retiming

Reduce the clock period


# Pipelining and Retiming

 


A pipeline register can cut a piece of combinational logic in smaller pieces. This reduces the  $T_{clk,min}$  for the entire design
 
# Retiming

- Sometimes, the partitioning is not nicely 50/50. In that case the benefit of pipeline registers to reduce  $T_{clk,min}$  is small, since the design has to be operated at the speed of the slowest stage



 - To maximize the benefit of the (pipeline) registers, they should be balanced so that each stage of combinational logic takes the same amount of logic delay



# Pipelining vs Retiming



- **Pipelining** is done by the designer, typically by rewriting HDL
- **Retiming** is done by the tools, during logic Synthesis

Of course, the designer can also rewrite the HDL


 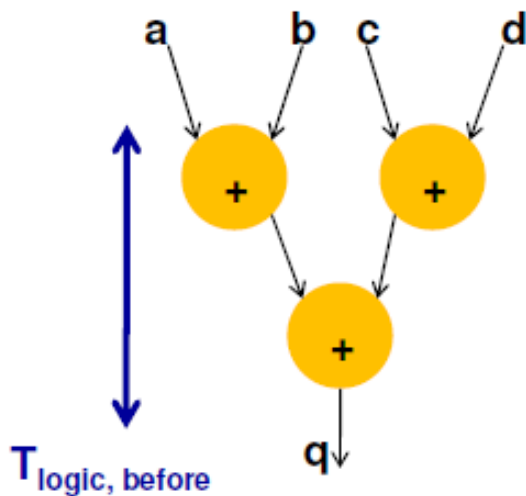
# Pipelining

- Cut a long combinational path in half by inserting a register
- Increases the latency cycle count of the design to get from the input to the output, you will need an extra clock cycle



# Rules for Consistent Pipelining...

- Assume a network of modules (combinational or sequential ) as follows.
- We will demonstrate how to move pipeline registers around while avoiding inconsistent pipelining




# ...Rules for Consistent Pipelining...



- You can add a register in front. It increases the latency of the network with one cycle, but the network will have the same functionality


# ...Rules for Consistent Pipelining...

 

- You can absorb a register at a single input if you recreate it at ALL the outputs of the module. This transformation will not change the latency nor the functionality of the network.

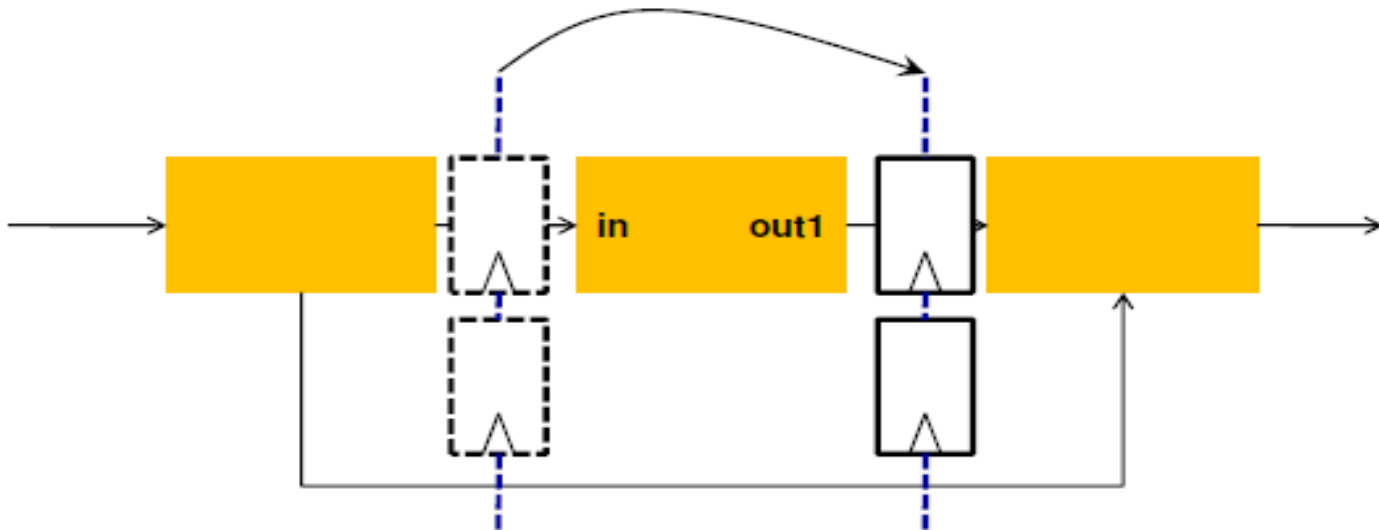
# ...Rules for Consistent Pipelining...

- Move it over another module – absorb register at the module inputs, recreate it to the module outputs




 
# ...Rules for Consistent Pipelining...

- Move it over the last module – absorb register at the module inputs, recreate it at the module output



# ...Rules for Consistent Pipelining...

All of these have the same behavior

  

# ...Rules for Consistent Pipelining...


- We can add multiple registers at the front ...





 
# ...Rules for Consistent Pipelining...

- and redistribute them using consistent pipelining




# ...Rules for Consistent Pipelining...

- Or...

 

 
# ...Rules for Consistent Pipelining...

**Tclk,min = 90ns**  
**Latency = 1 cycle**  
**Throughput = 1 / cycle**




 **Tclk,min = 30ns**  
**Latency = 3 cycles**  
**Throughput = 1 / cycle**


 
# ...Rules for Consistent Pipelining...


- Following these rules, you'll find that you cannot pipeline loops (i.e. increase the number of registers in a feedback path)



**There is a single register  
in this path**

 
# ...Rules for Consistent Pipelining...

- To pipeline, add a register at the front



 
# ...Rules for Consistent Pipelining...

- To move the pipeline register to the module output, ALL the inputs need to absorb a register


 
# ...Rules for Consistent Pipelining...

- In the resulting network, there is still only one register in the loop




- **Part 2 – Hardware architectures (Block ciphers and Hash Function)**




# Basic Architectures

- There are four types of architectures about bloc ciphers
  - Iterative architecture
    - Use only one round
  - Partial loop unrolling
    - Use more rounds
  - Loop unrolling
    - Use all rounds (Outer-round pipelining)
  - Use inner- and outer-round pipelining


# Iterative architecture

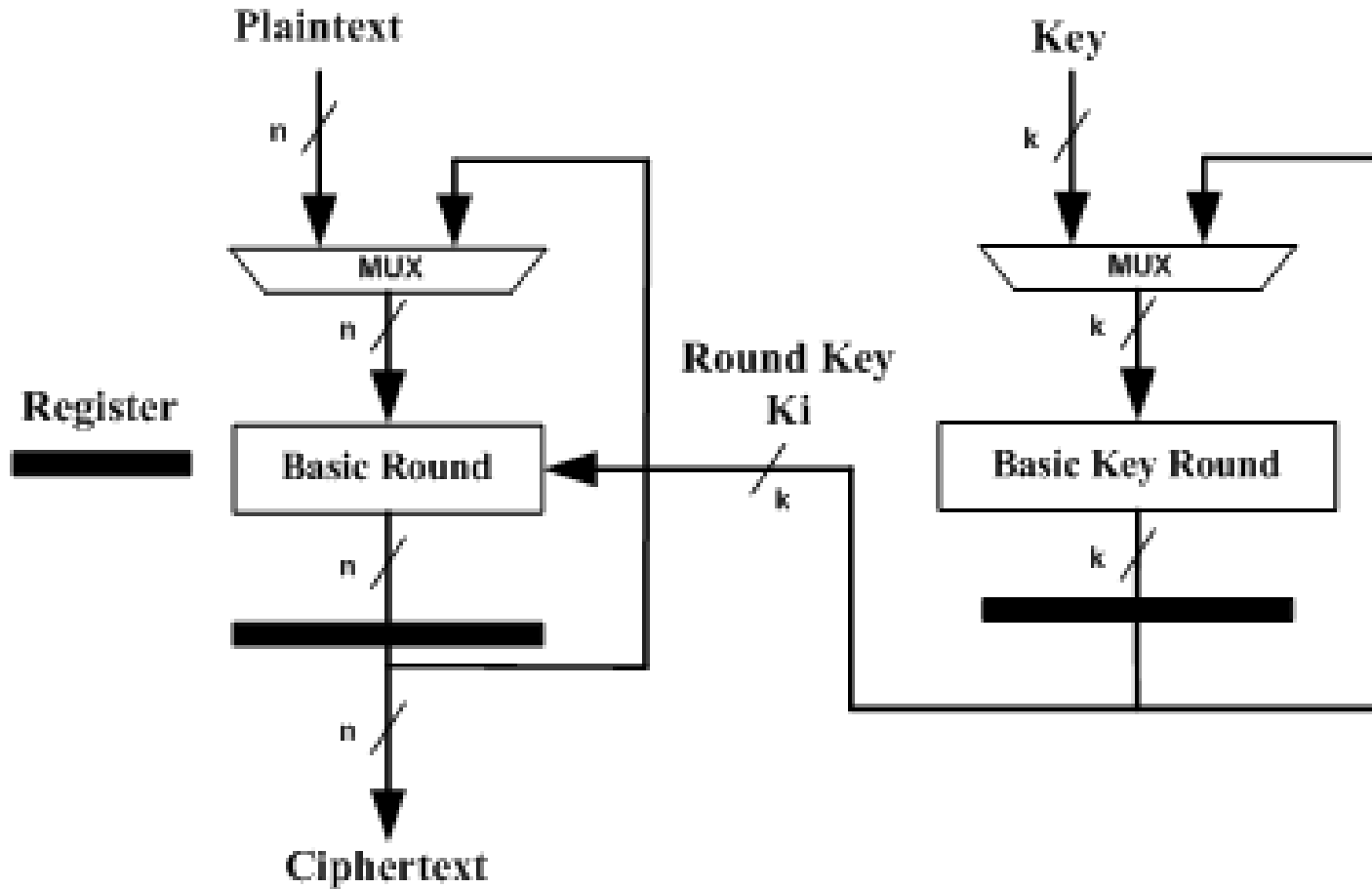


# Partial loop unrolling

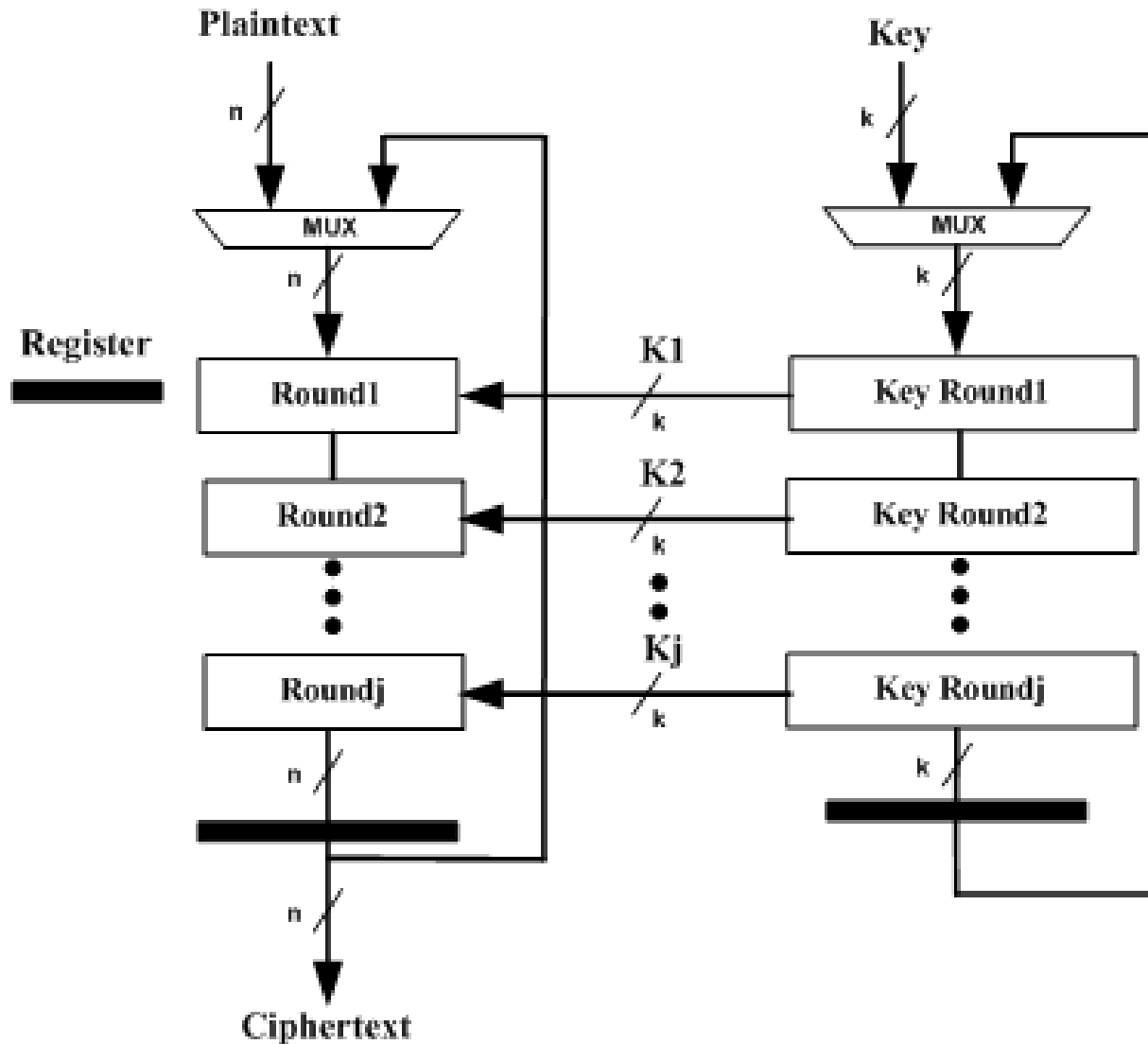

# Loop unrolling

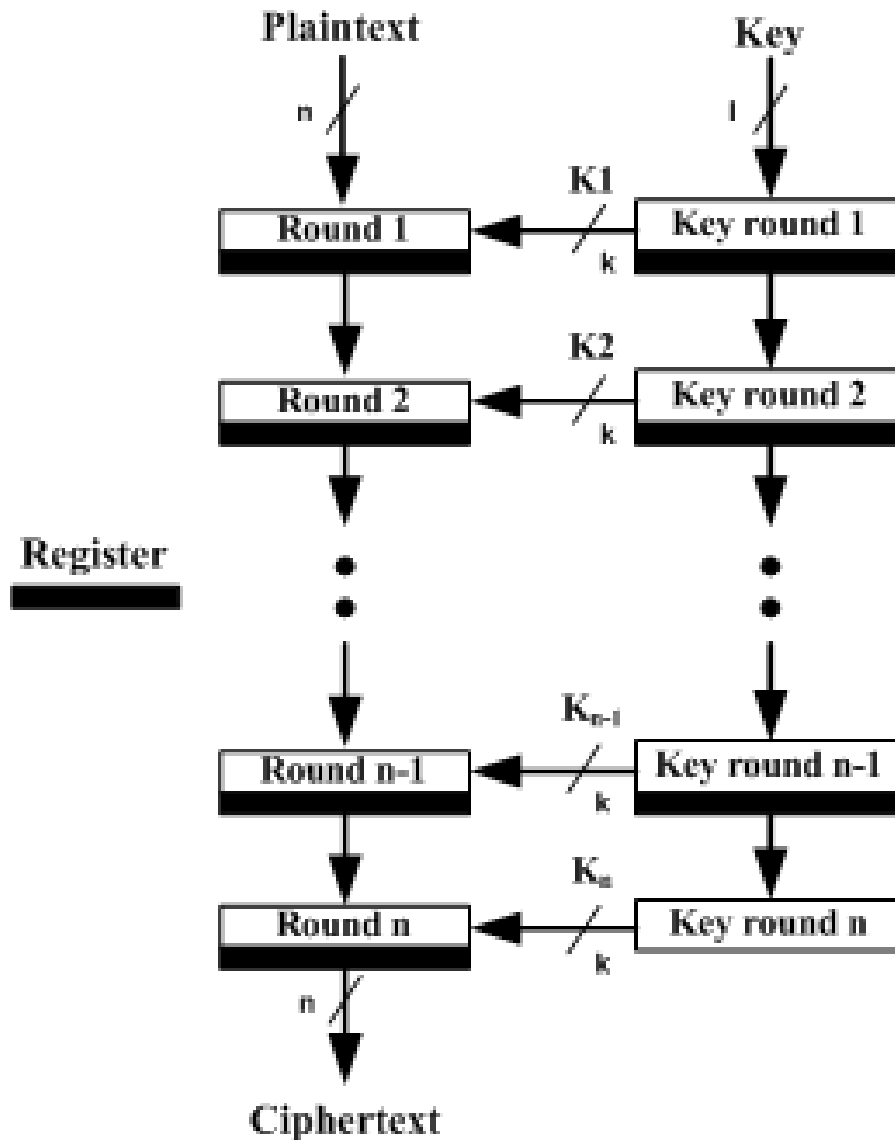


# Inner- and outer-round pipelining...

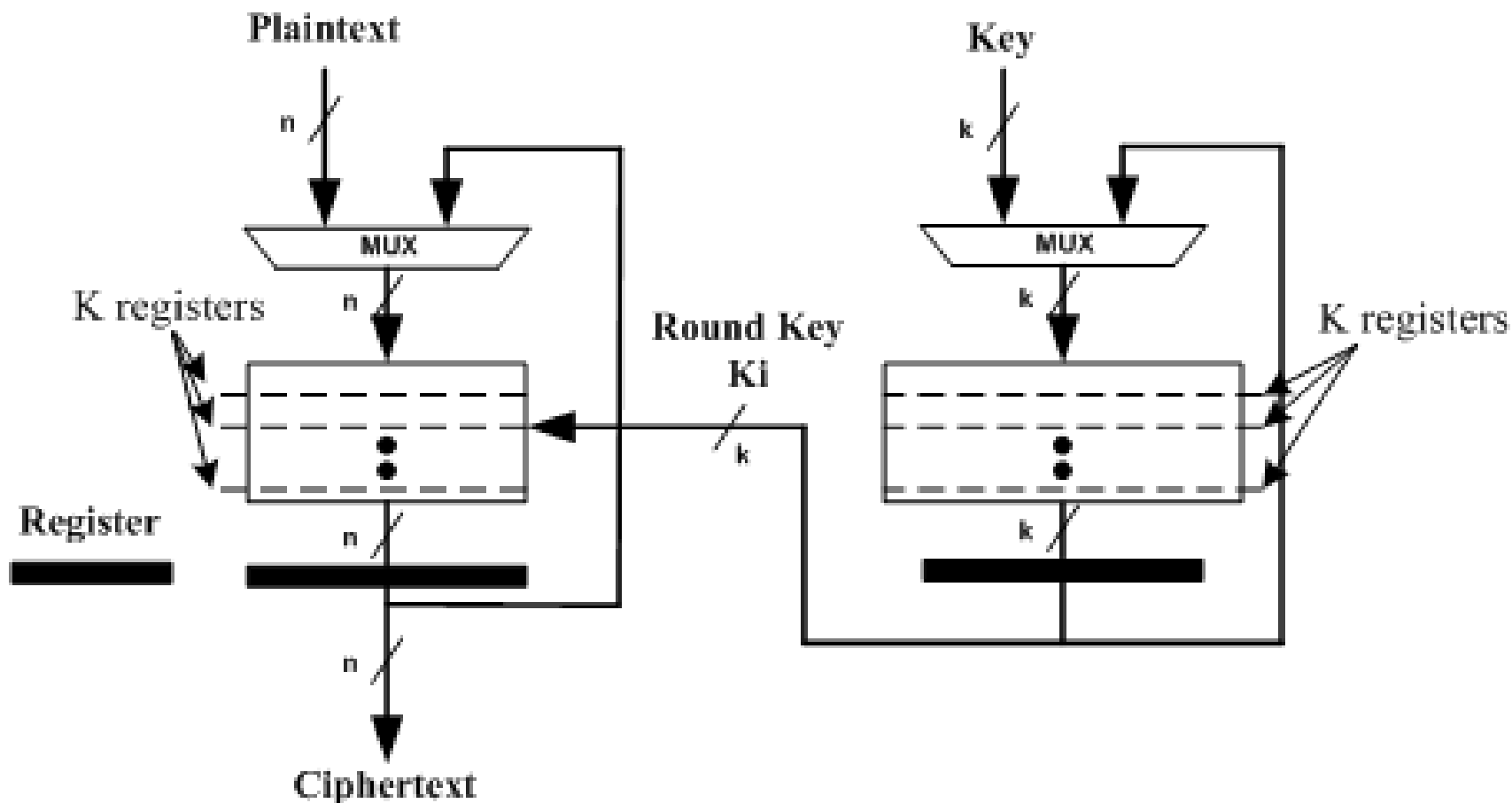


*Total # of pipeline stages = #rounds · K  
(K=1)*

# ...Inner- and outer-round pipelining

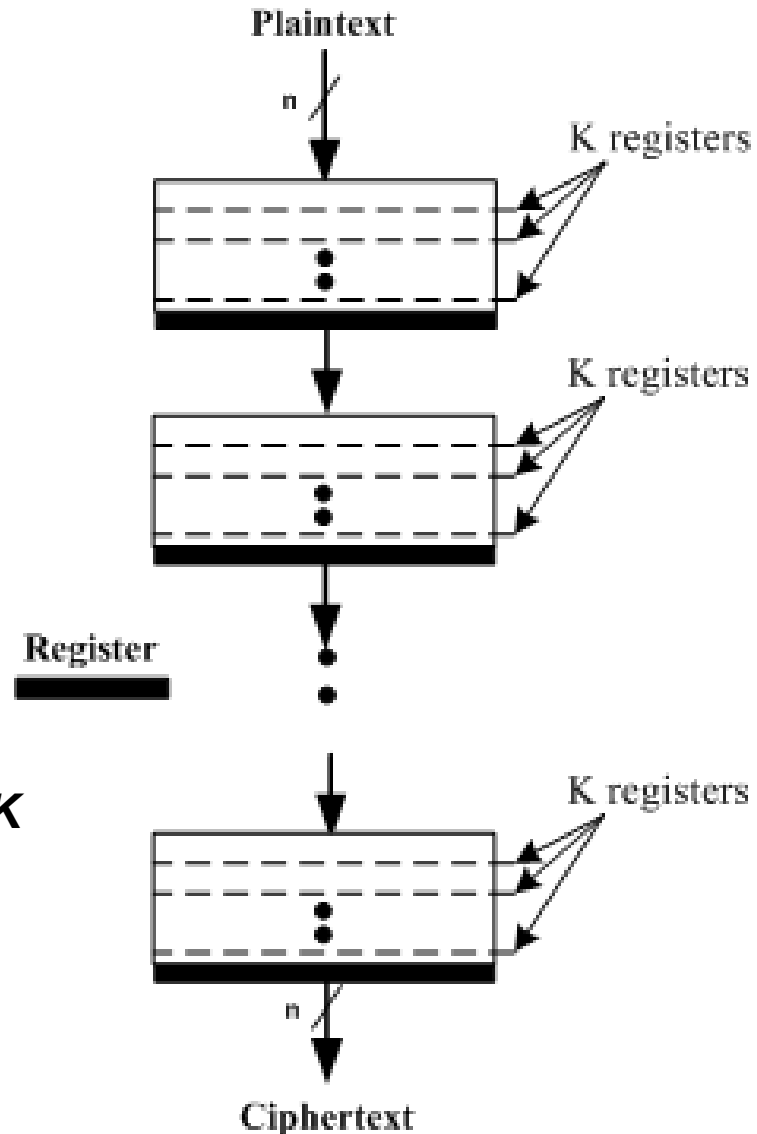


***Total # of pipeline stages = #rounds · K***

# Partial loop unrolling example: DES

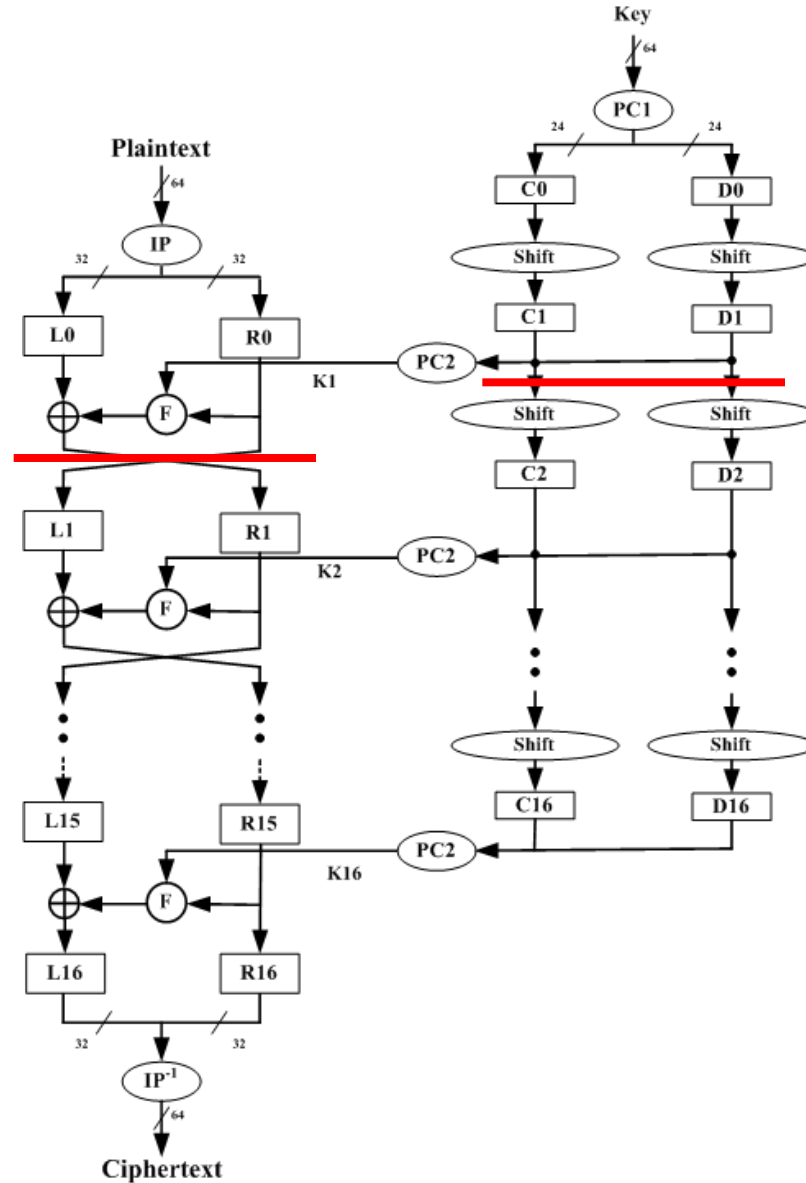

register

# ...DES...

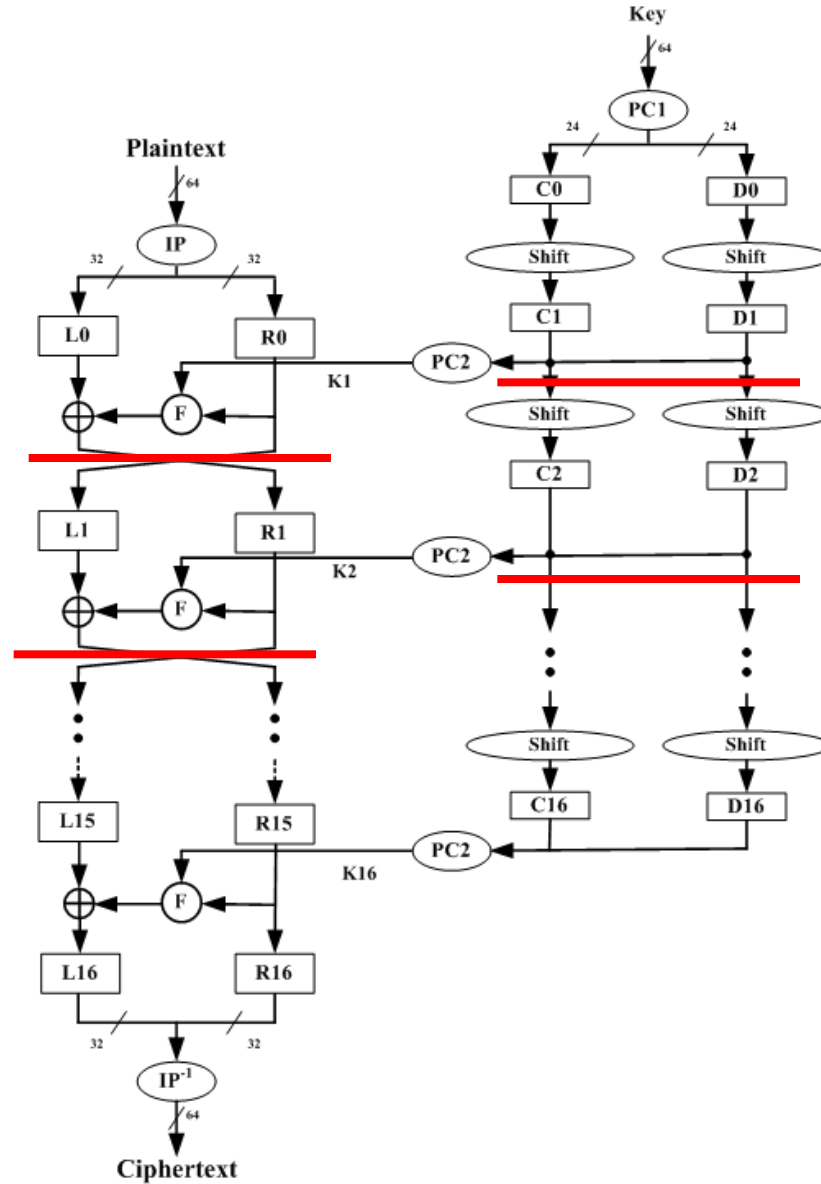


register






# ...DES

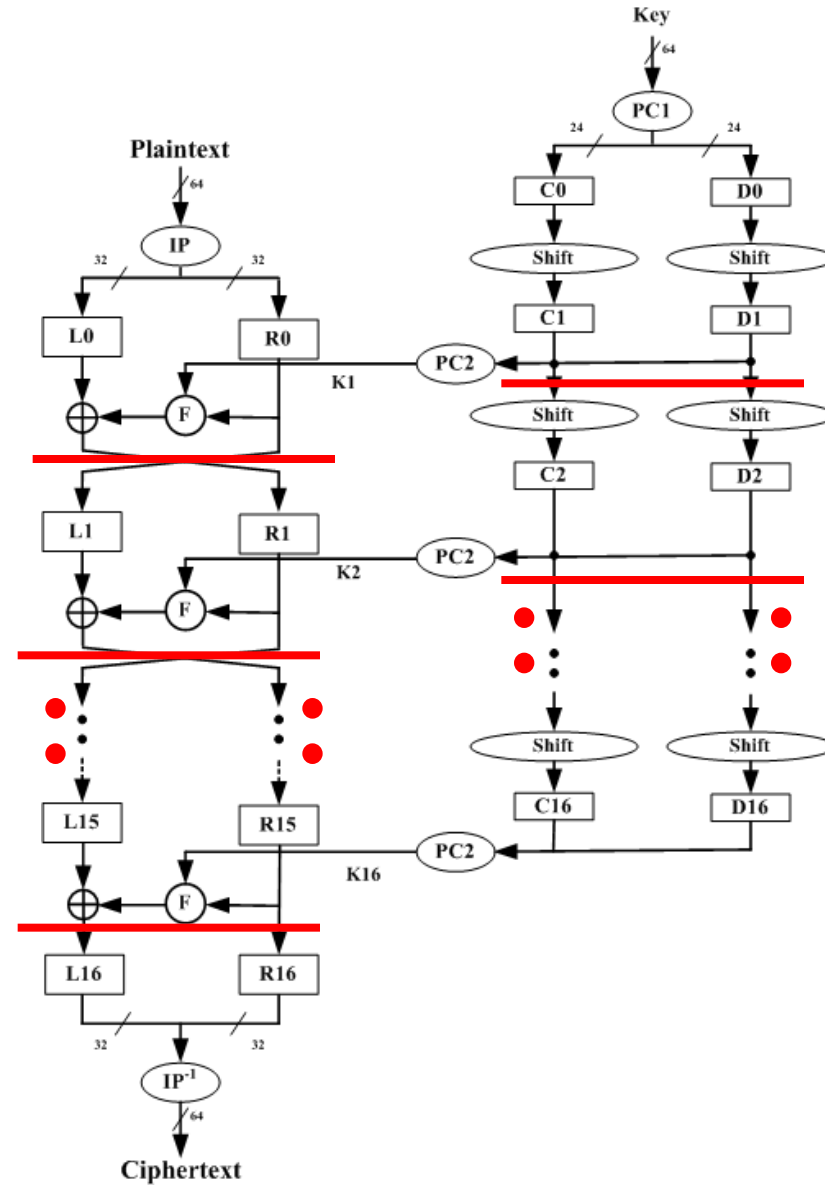


register


# Triple-DES

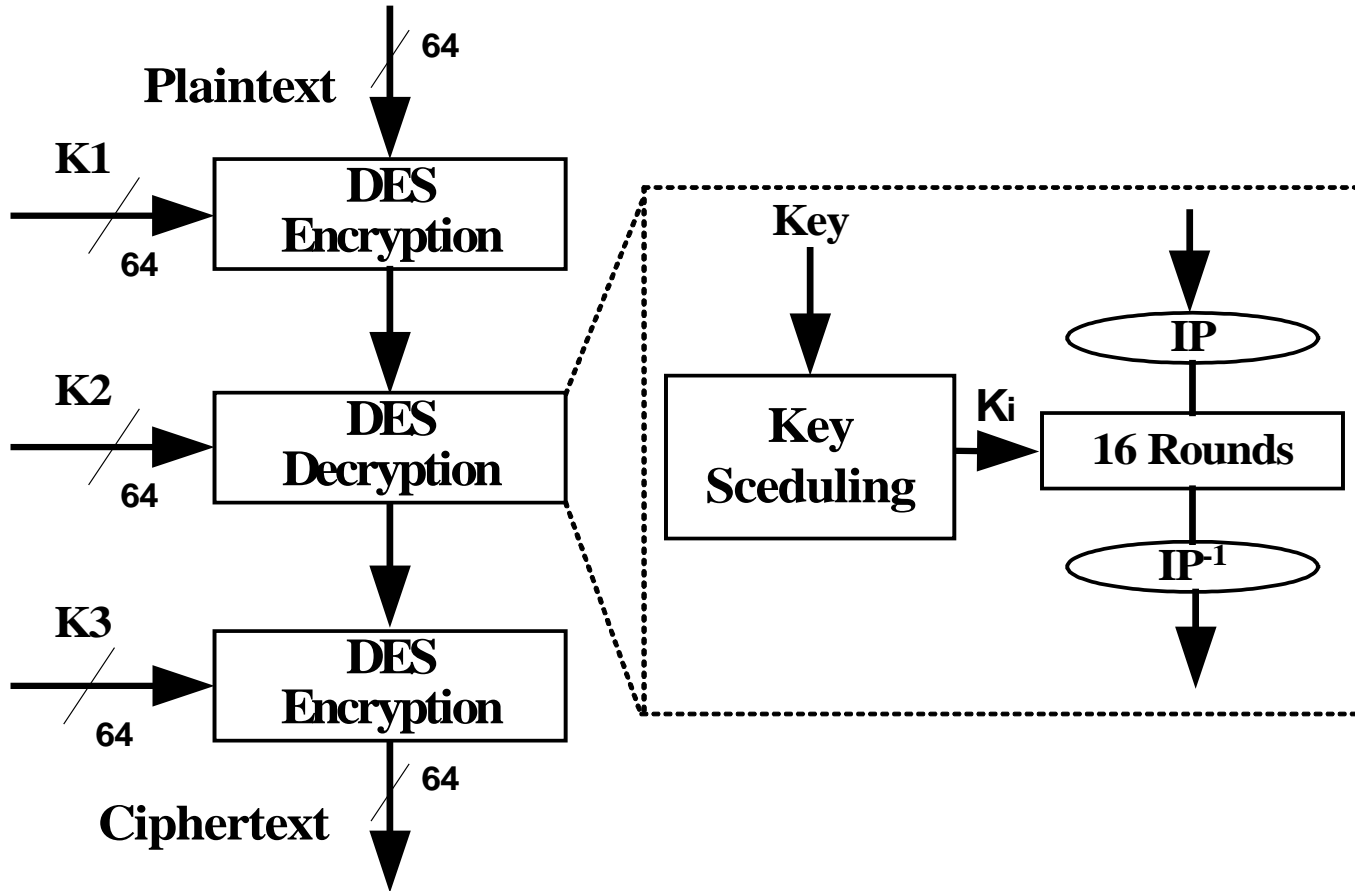


# Triple-DES: Iterative architecture

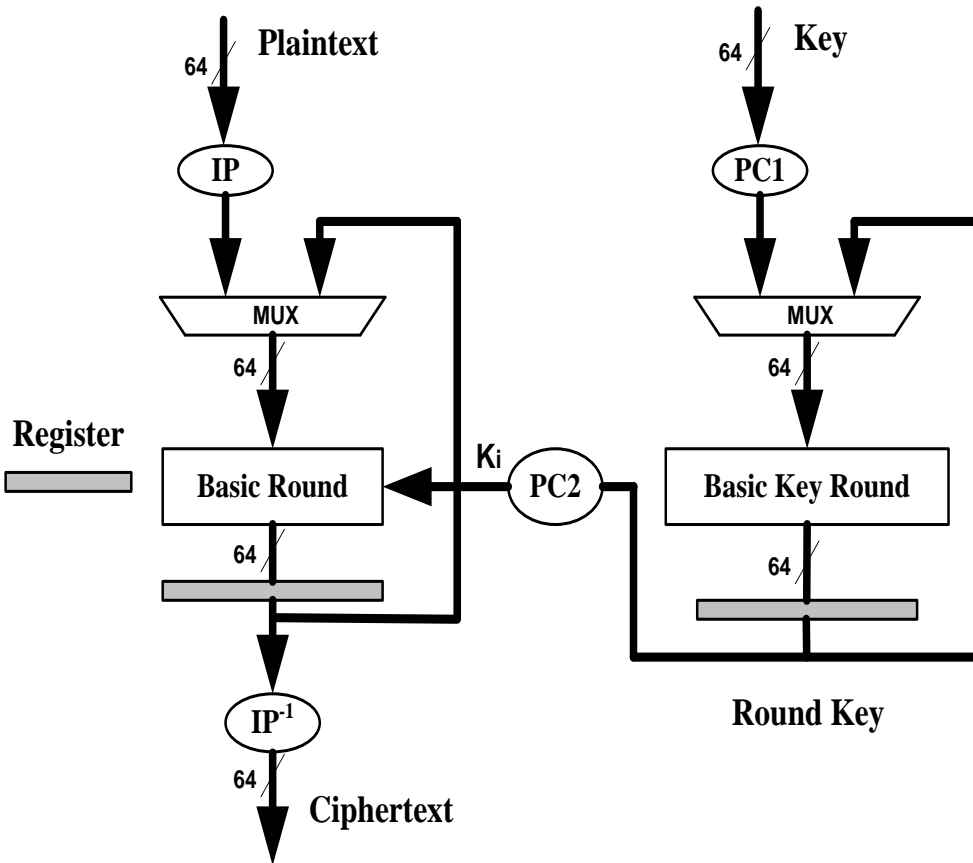

# Triple-DES: Partial loop unrolling

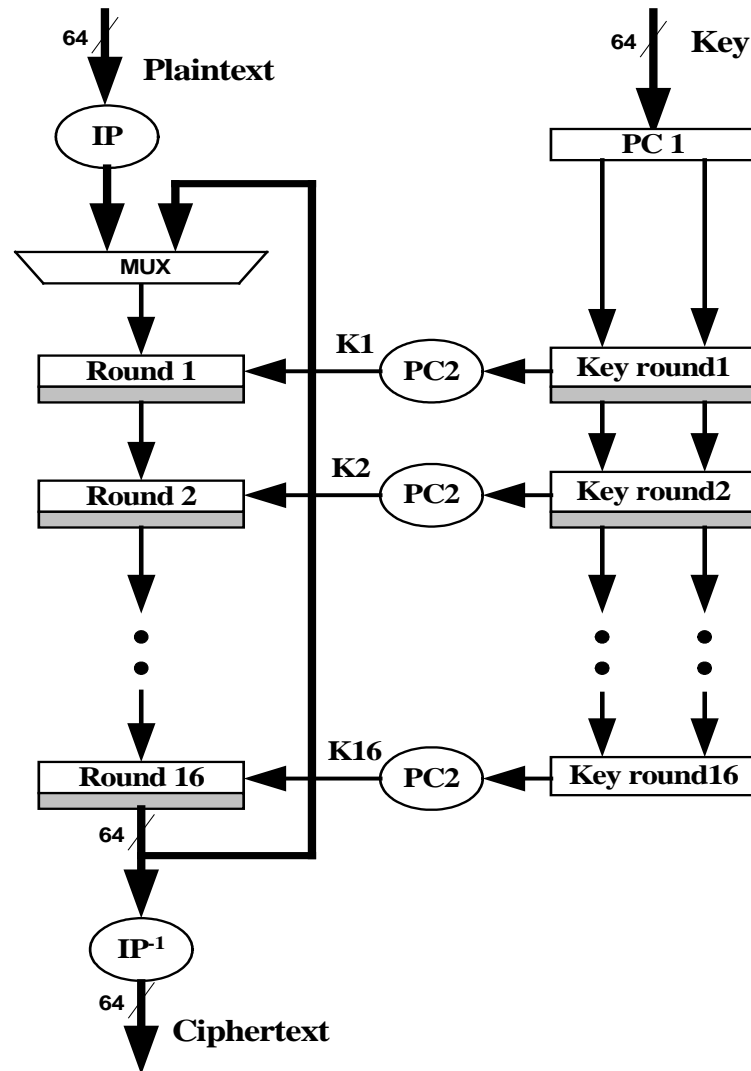

# Triple-DES: Loop unrolling

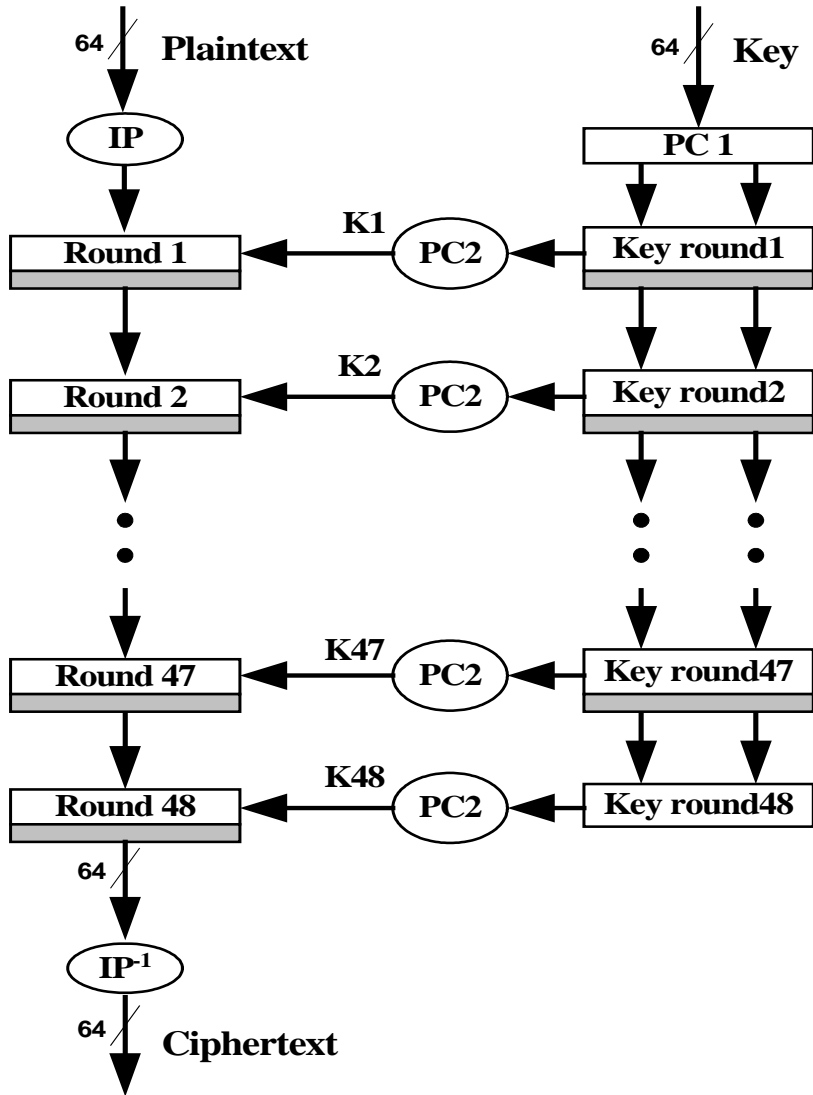

# KASUMI Block Cipher Application

KASUMI block cipher is used:





- In new GSM encryption algorithm A5/3
- In 3G and 4G, f8 and f9 algorithms
- In Transport Layer Securities (TLS)

# KASUMI Block Cipher...


- Is the 64-bit block cipher
- Is a Feistel block cipher with 8 rounds
- The odd rounds have different structure than even rounds
- Uses 64-bit plaintext/ciphertext and 128-bit key




# ...KASUMI Block Cipher

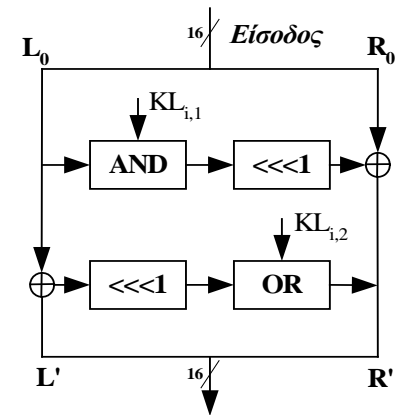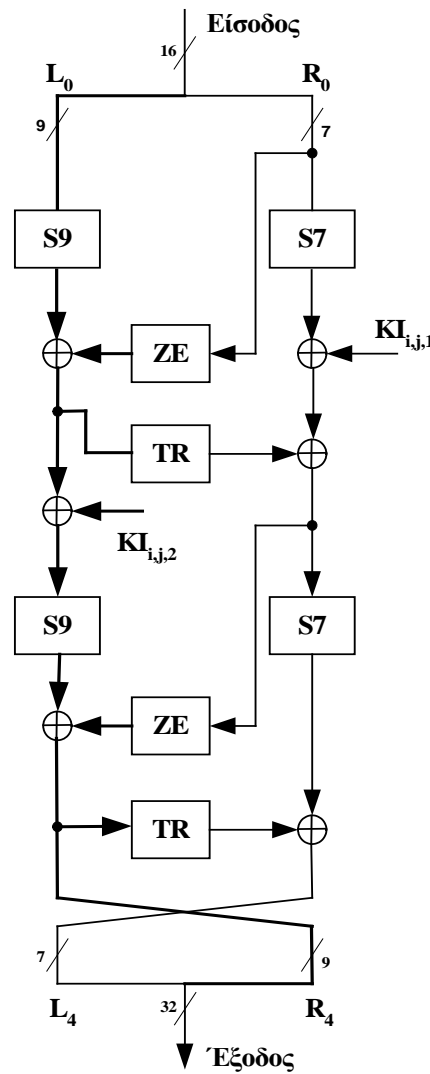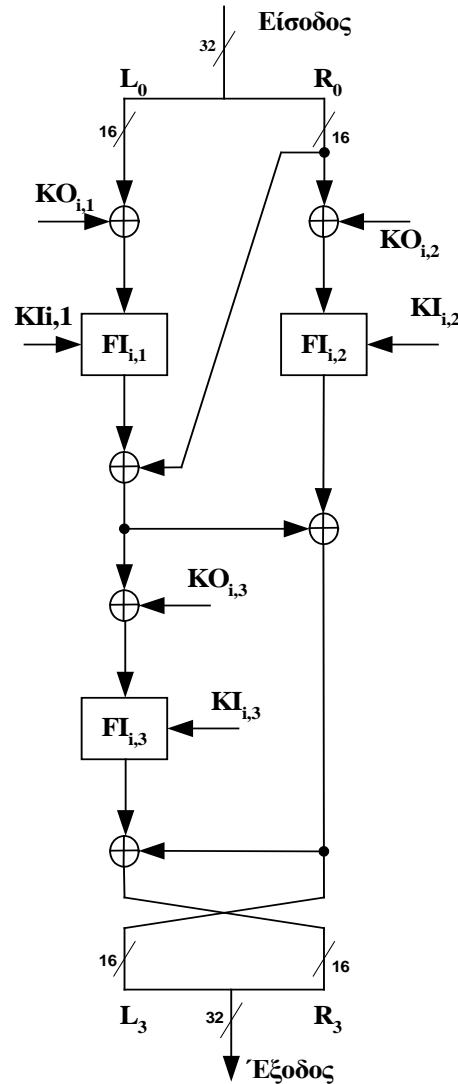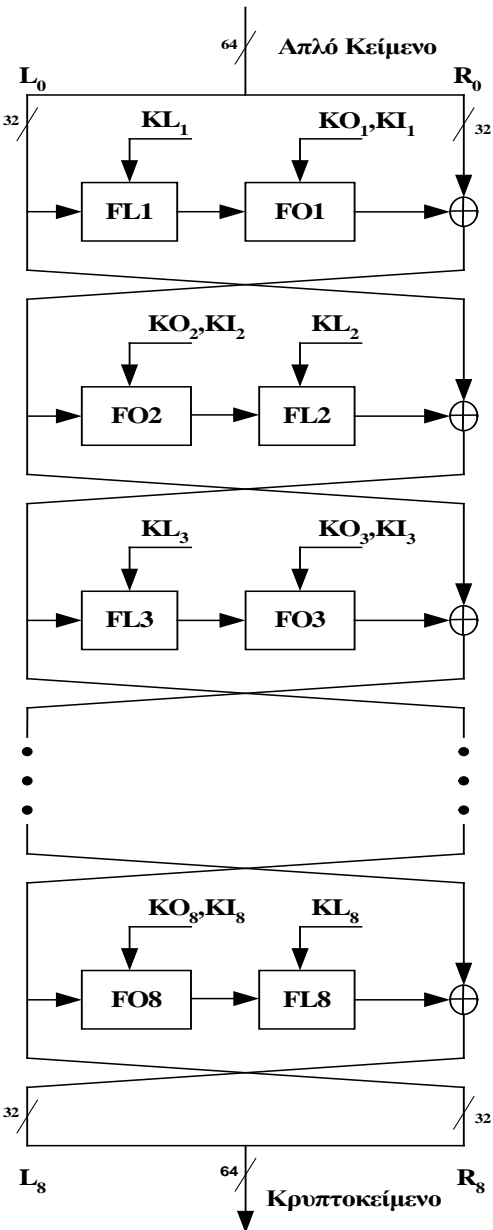


# KASUMI Key Scheduling

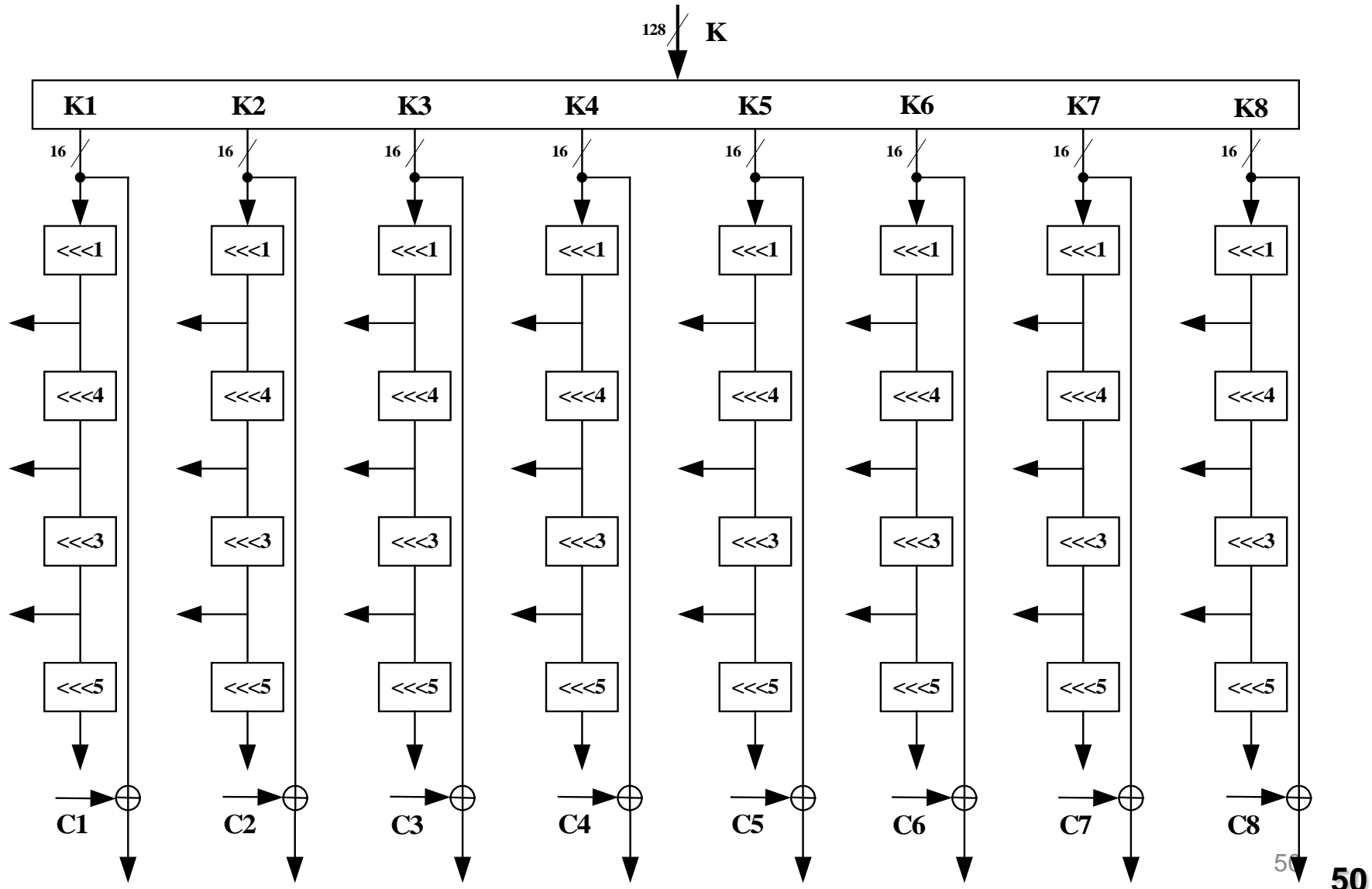


# KASUMI: Partial loop unrolling

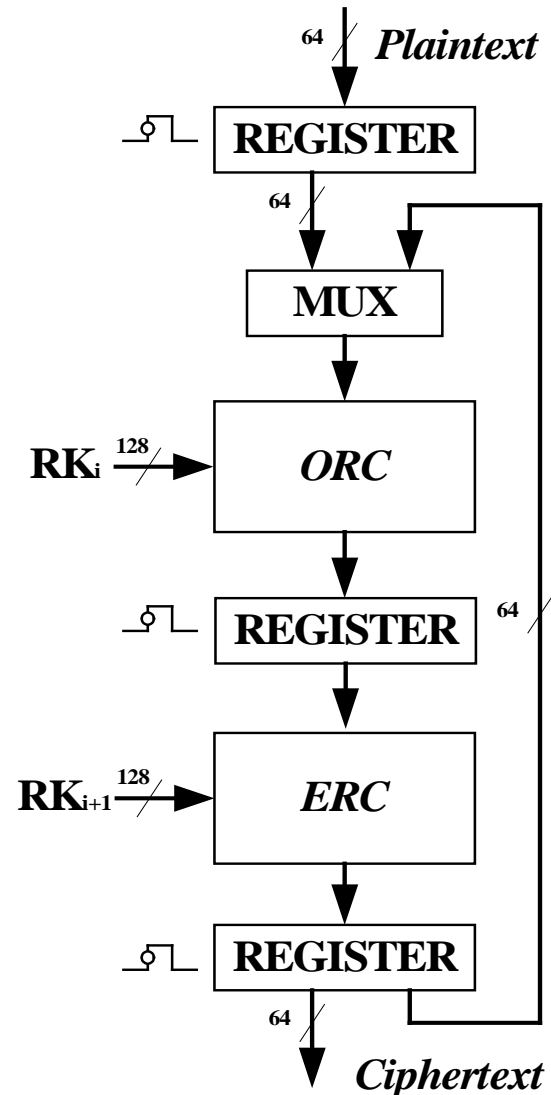

# KASUMI: Loop unrolling

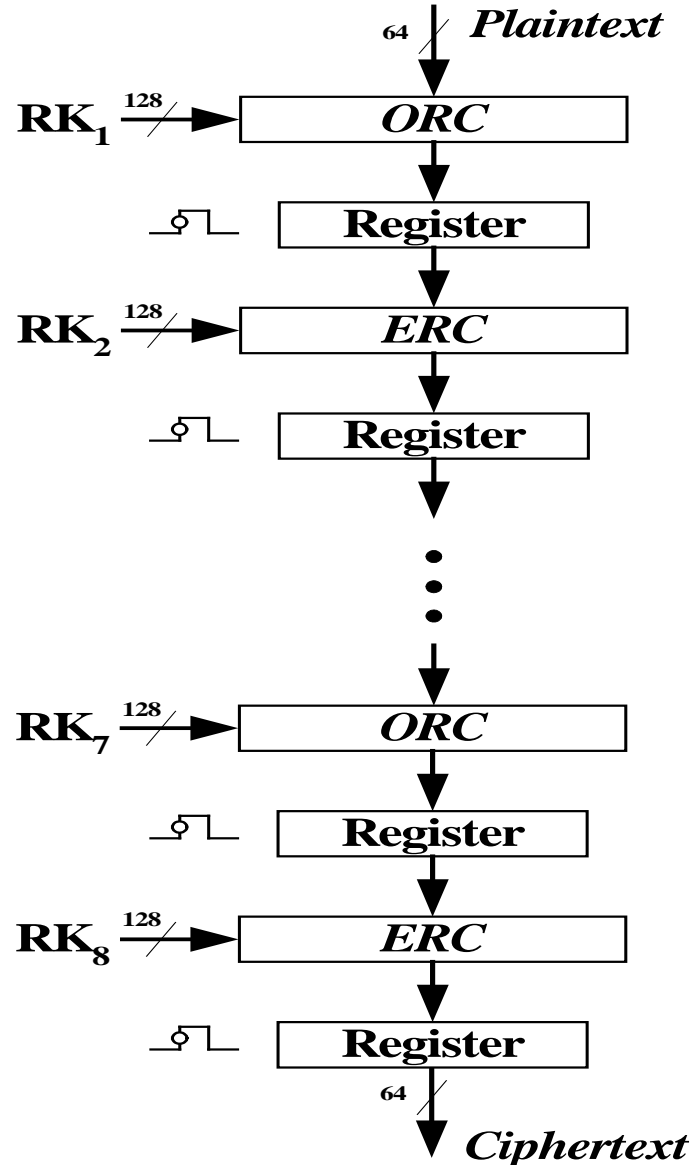


# Round Implementation

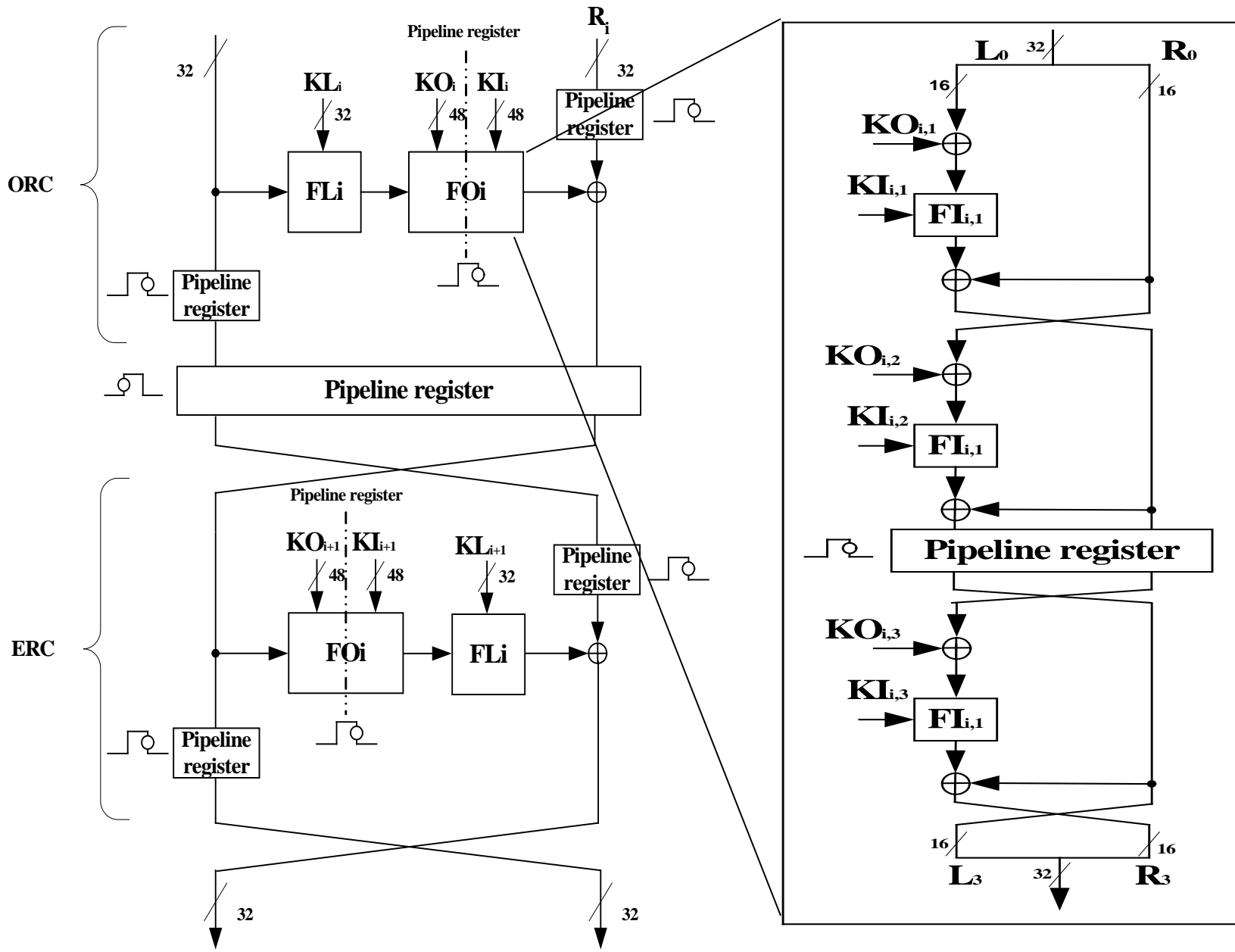

# Whirlpool Hash Function

- Endorsed by European NESSIE project
- Uses modified AES internals as compression function
- Addressing concerns on use of block ciphers seen previously

# Whirlpool Overview

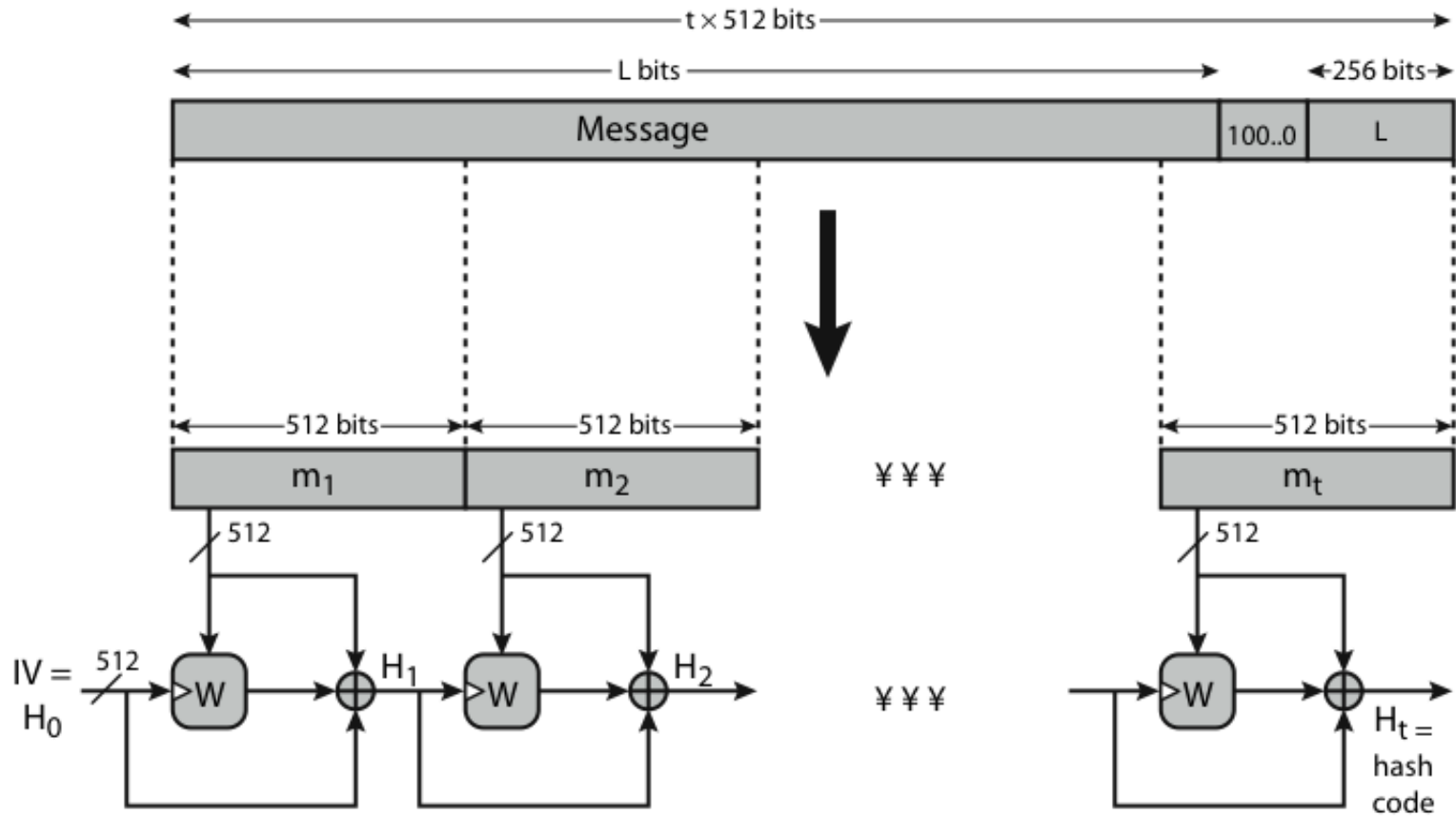


Note: triangular hatch marks key input

# Whirlpool Block Cipher W


- Designed specifically for hash function use
- With security and efficiency of AES
- But with 512-bit block size and hence hash
- Similar structure & functions as AES but
  - input is mapped row wise
  - has 10 rounds
  - uses different S-box design & values



# Whirlpool Block Cipher W

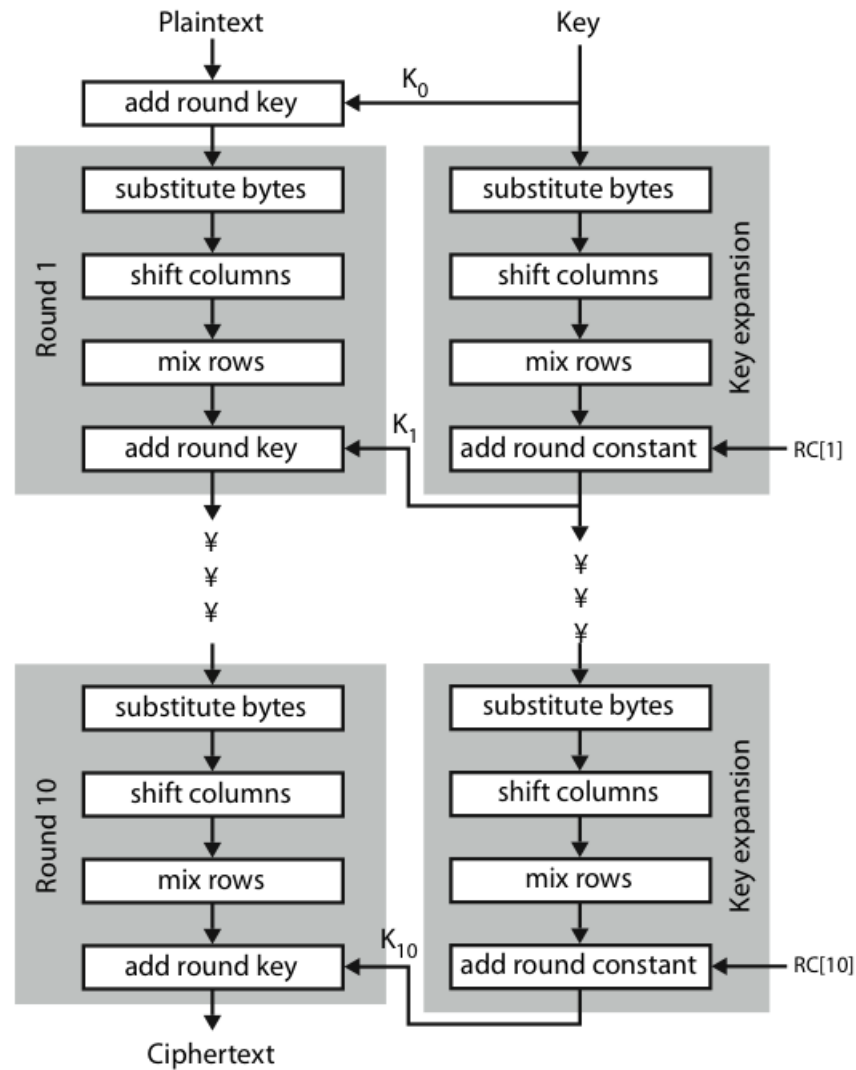


# Whirlpool Architecture...

 


- The Padder pads the input data and converts them to  $(n+256)$ -bit padded message
- An interface with 256-bit input for Message is considered
- The  $n$ , specifies the total length of the message

# ...Whirlpool Architecture...

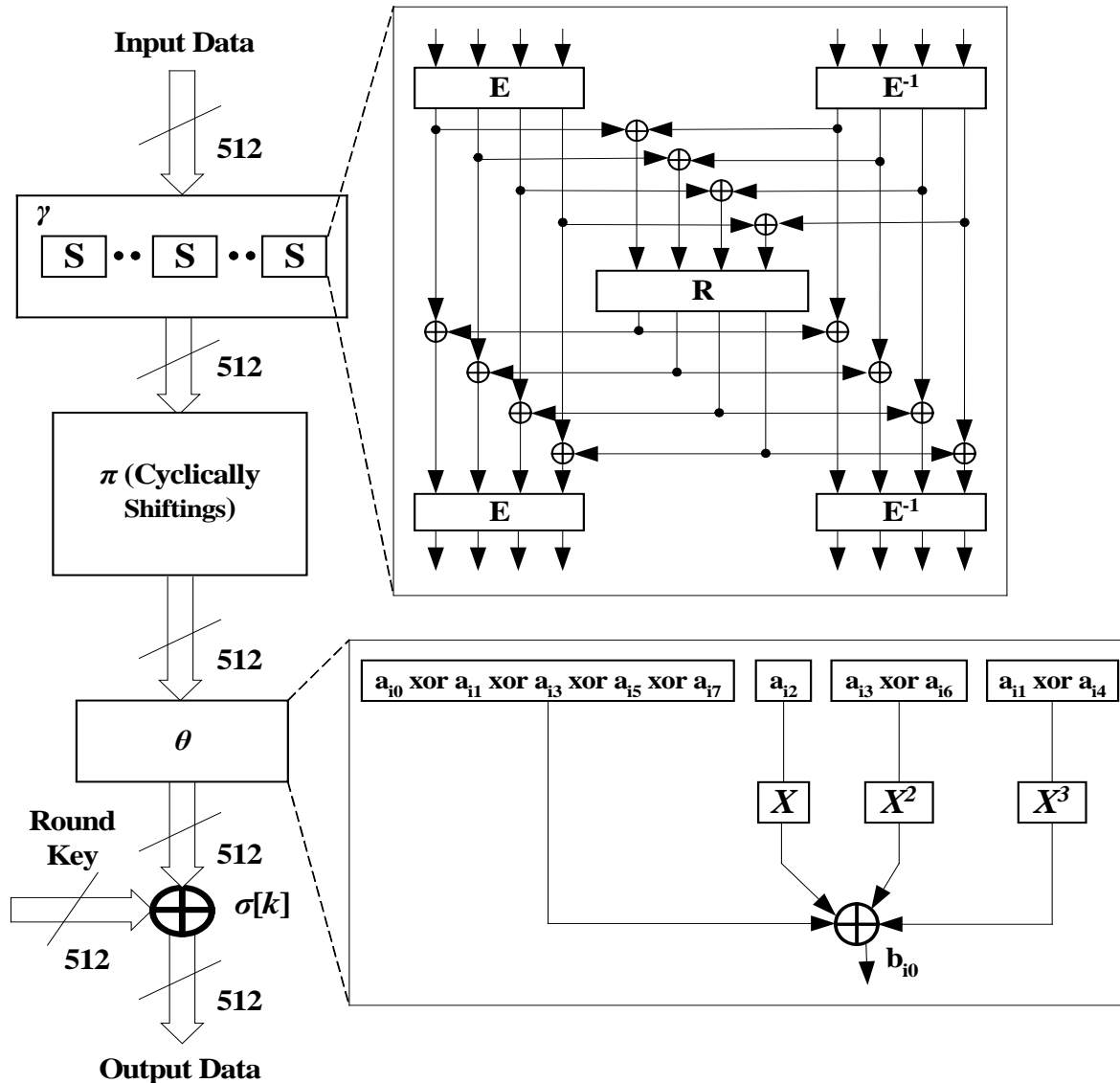

# ...Whirlpool Architecture

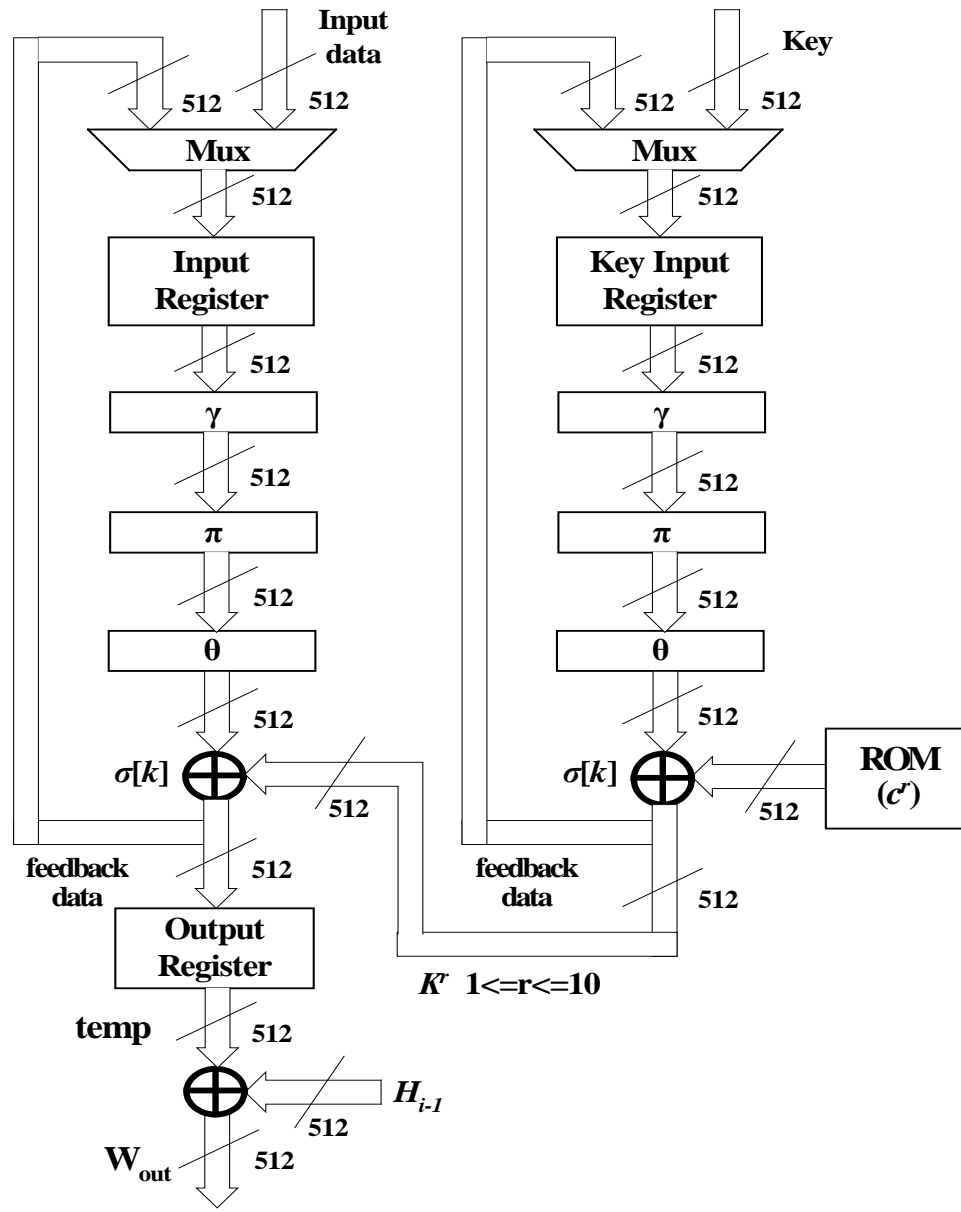

- This implementation has two similar parallel datapaths, the data randomizing and the key schedule
- The input block  $m_i$  is set to the Input data simultaneously with the initial vector (IV) to the Key
- In a clock cycle, one execution round is executed and, simultaneously, the appropriate round key is calculated.
- Latency = 10 clock cycles

Questions??